



alllabexperiments.com

Observations:

DC balance:

SNO.		S( $\Omega$ )	P( $\Omega$ )	Q( $\Omega$ )	R( $\Omega$ )	
					L <sub>1</sub>	L <sub>2</sub>
1.	C <sub>1</sub> = 0.1 $\mu$ F	0.1	1000	1000	40	69
2.	C <sub>2</sub> = 0.2 $\mu$ F	0.1	1000	1000	44	70

AC Balance:

	C = 0.1 $\mu$ F		C = 0.2 $\mu$ F	
	R	M	R	M
For L <sub>1</sub>	40	5600	44	2300
For L <sub>2</sub>	69	6500	70	3100
For L <sub>3</sub>	105	6540	105	3000

Aim: To determine the self inductance  $L$  of the given coil by Anderson's bridge.

Apparatus:

Anderson's bridge, headphones & connecting wires.

[alllabexperiments.com](http://alllabexperiments.com)

Theory:

In the diagram,  $C$  is a fixed standard capacitor,  $P, Q, R, S$  and  $\pi$  are resistances  $e$  is an audio oscillator and  $H$  is a headphone.

The condition for balance is that the potential at  $D$  &  $E$  are the same. Under this condition, no current flows through the path  $DE$ .

The potential drop along  $ABC =$  potential drop along  $ADC$ . Hence, from the figure,  $i_1 P + (i_1 + i_2) Q = i_3 (R + j\omega L + S')$  — (1)

Here,  $S' = S + R_L$  where  $R_L$  is the resistance of the coil.

For the mesh  $ABEA$ :

$$i_1 P - i_2 (\pi + \frac{1}{j\omega C}) = 0 \quad \text{--- (2)}$$

The potential difference from  $A$  to  $E$  is equal to that from  $A$  to  $P$  as no current flows through the headphone for the balance.

$$\text{Thus, } \frac{i_2}{j\omega C} = i_3 R \quad \text{--- (3)}$$

Substituting  $i_3$  from (3) into (1),

$$i_1 (P + Q) = \frac{1}{j\omega CR} i_2 [R + S' + j\omega L] - i_2 Q$$

$$i_1 (P + Q) = i_2 \left[ \frac{R + S' + j\omega L - Q}{j\omega CR} \right] \quad \text{--- (4)}$$



calculations:

for  $L_1$ :

$$1) L_0 = CR (\omega + 2\pi)$$

$$= 0.1 \times 10^{-6} \times 40 [1000 + 2 \times 5600]$$

$$= 48.8 \text{ mH}$$

$$2) L = 0.2 \times 10^{-2} \times 44 [1000 + 2 \times 2300]$$

$$= 49.28 \text{ mH}$$

$$\text{mean } L_1 = \frac{L_0 + L}{2} = \frac{48.8 + 49.28}{2} = 49.04 \text{ mH}$$

[alllabexperiments.com](http://alllabexperiments.com)

for  $L_2$ :

$$1) L_0 = 0.1 \times 10^{-6} \times 69 [1000 + 2 \times 6500]$$

$$= 96.6 \text{ mH}$$

$$2) L = 0.2 \times 10^{-6} \times 70 [1000 + 2 \times 3100]$$

$$= 100.8 \text{ mH}$$

$$\text{mean } L_2 = \frac{96.6 + 100.8}{2} = 98.7 \text{ mH}$$

for  $L_3$ :

$$1) L_0 = 0.1 \times 10^{-6} \times 105 (1000 + 2 \times 6540)$$

$$= 147 \text{ mH}$$

$$2) L = 0.2 \times 10^{-6} \times 105 (1000 + 2 \times 3,000)$$

$$= 147 \text{ mH}$$

$$\text{mean } L_3 = 147 \text{ mH}$$

Eliminating  $i_1$  &  $i_2$  with the help of (2) & (4), by equating the imaginary parts:

$$S' = \frac{RQ}{P}$$

This is the condition of DC balance of the bridge.

[alllabexperiments.com](http://alllabexperiments.com)

Equating the real parts, we get

$$L = CR \left( \frac{P\alpha + Q\alpha + P\alpha}{P} \right)$$
$$= C \left( R\alpha + \frac{RQ\alpha + RQ\alpha}{P} \right)$$

Substituting,

$$L = C [R\alpha + S'\alpha + RQ]$$
$$\text{or } L = C [RQ + \alpha(R + S')]$$

The values of  $C, R, Q, S'$  and  $\alpha$  at the balance condition give us self inductance  $L$  of the coil. If the resistances are in  $\Omega$  & capacitance is in Farads, then  $L$  is in Henry.

Precautions & Sources of Error:

1. A fractional resistance box can be used in series with  $P$  to get the exact balance point.
2. The capacitance should not have an appreciable leakage & should be of low value of capacity.

Result:

The value of inductance  $L_1, L_2$  &  $L_3$  are  $49.04$ ,  $98.7$  mH &  $147$  mH