 


## EXPERIMENT-7

AIM:- To study the I-V characteristics of the Common Source (CS) configuration of FET.

Apparatus:- Variable d.c. regulated power supply, milliammeter (0-20mA), Voltmeter (0-20V) and (0-2V), resistors and FET.



<https://alllabexperiments.com>

# EXPERIMENT-7

IM 2-

To study the I-V characteristic of the Common Source (CS) configuration of FET.

Apparatus:- Variable d.c regulated power supply, milliammeter (0-20 mA), voltmeters (0-20V), (0-2)V, resistors and FET.

Theory:- The Field Effect Transistor (abbreviated as FET) is a three terminal unipolar semiconductor device in which current is controlled by an electric field. The basic structure of JFET is shown in fig. on the opp. page. There are two terminals.

- ① Source
- ② Drain
- ③ Gate

<https://alllabexperiments.com>

Standard Notations worth notings FET are as follows:

- ① SOURCE:- The terminal through which the majority carriers enter the channel, is called the source terminal S and the conventional current entering the channel at S is denoted by  $I_s$ .
- ② DRAIN:- The terminal through which the majority carriers leave the

channel is called the drain terminal D and the conventional current leaving the channel at D is designated as  $I_D$ .

③ Gate<sup>g</sup>- There are two internally connected heavily doped impurity regions formed by alloying  $g$  by diffusion or by any other method available to create two p-n junctions. These impurity regions are called the gate G. A voltage  $V_{GS}$  is applied between the gate and source in the direction to reverse-bias the p-n junction.

④ Channel<sup>c</sup>- The region between the source and the drain, sandwiched between the two gates is called the channel and the majority carriers move from the source to drain through this channel.

<https://alllabexperiments.com>

## CHARACTERISTICS of FET 2-

There are two types of static characteristics


① Output or Drain

② Transfer

In the common source configuration, the bias voltages are applied b/w the gate and source and drain and source. Now, we discuss the characteristic curve for common source configuration.

Teacher's Signature : \_\_\_\_\_

<https://alllabexperiments.com>

 

FAMILY OF V-I CHARACTERISTICS OF JFET

## Output or Drain Characteristics :-

The curve drawn between drain current  $I_D$  and drain-source voltage  $V_{DS}$  with gate to source voltage  $V_{GS}$  as the parameter is called the drain curve.

It is observed from the graph that as a negative gate bias voltage is increased

(i) the maximum saturation drain current becomes smaller because the conducting channel becomes narrower.

(ii) Pinch-off voltage is reached at lower value of drain current  $I_D$  than when  $V_{GS} = 0$ .

When  $V_{GS} = 0$ , the drain current  $I_D$  inc.

linearly for small applied voltage  $V_{DS}$ . With the inc. in drain current  $I_D$ , the

ohmic voltage drop across source and the channel region reverse-biases the

gate junction. and this reverse-biasing is more at the drain end than the source end. so with the inc. in  $V_{DS}$



the conducting portion of the channel begins to constrict more than at the

drain end. Eventually a voltage  $V_{DS}$  is reached at which the channel is pinched

off. The  $I_D$  current no longer inc. with the inc. in  $V_{DS}$ . It reaches a constant saturation value.

# TRANSFER CHARACTERISTICS:

<https://alllabexperiments.com>

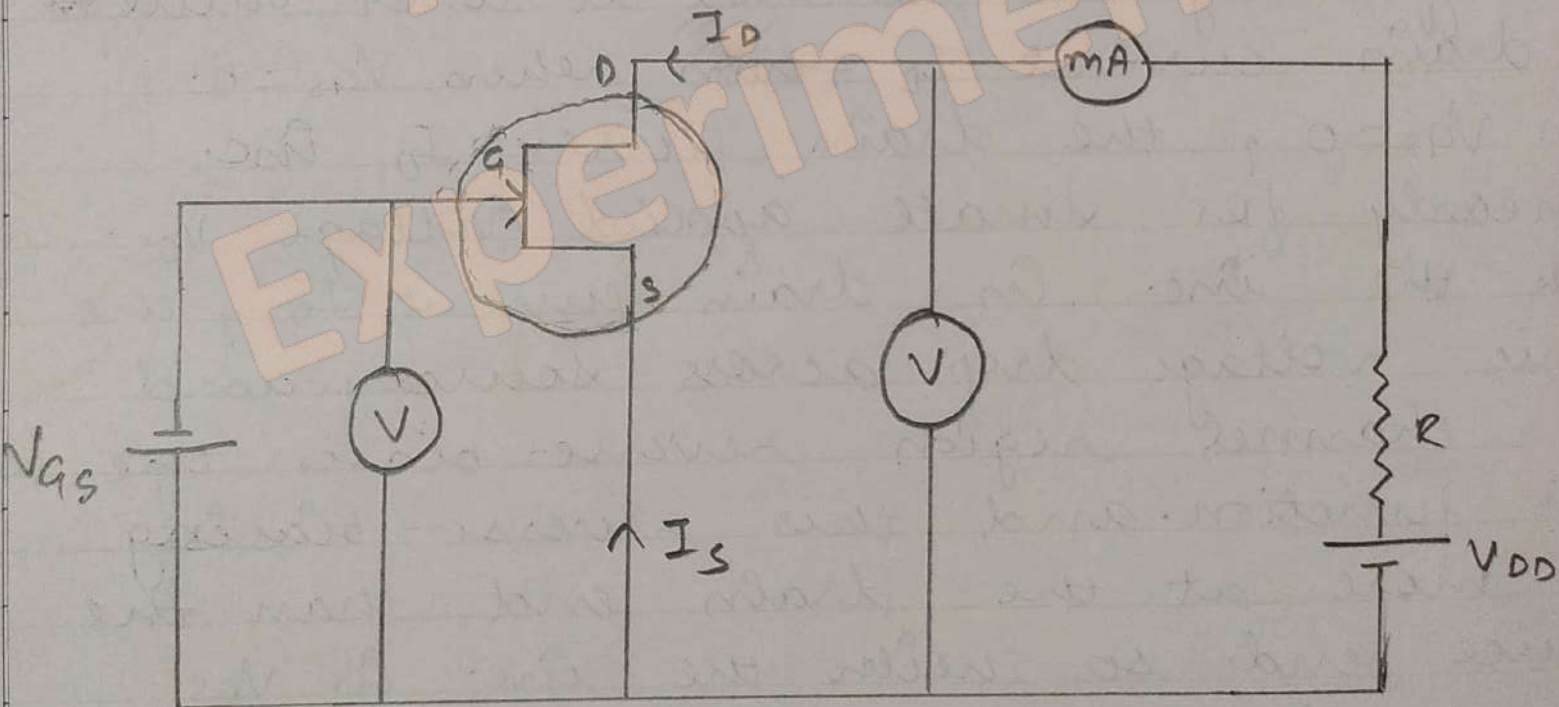 


Scale

x-axis 1 div = 0.05

y-axis 1 div = 0.05

<https://alllabexperiments.com>

 

TRANSFER CHARACTERISTICS :- The transfer characteristics for JFET can be determined experimentally by keeping drain source voltage  $V_{DS}$  constant and determining drain current  $I_D$  for various values of gate-source voltage  $V_{GS}$ . The curve so plotted is shown in fig on opp. page. It is observed that :-

- (i) Drain current  $I_D$  decreases with the increase in -ve gate-source voltage.
- (ii) drain current  $I_D = I_{DSS}$  when  $V_{GS} = 0$
- (iii) drain current  $I_D = 0$  when  $V_{GS} = V_p$ .

PROCEDURE :-

<https://alllabexperiments.com>

- ① Connect the circuit as shown:
- ② fix the gate to source voltage  $V_{GS}$  to some suitable value.
- ③ Vary  $V_{DS}$  and note down  $V_D$  and  $I_D$
- ④ Now change the value of  $V_{GS}$  and repeat step ③.
- ⑤ Now plot  $I_D$  versus  $V_D$  and trace the curve. The curve obtained is the output/drain characteristic of Common Source FET.
- ⑥ Now fix  $V_{DS}$  constant to some suitable value.
- ⑦ Vary  $V_{GS}$  and note down voltage  $V_G$  and




S.No	$V_{DS} = 1.0V$		$V_{DS} = 2V$	
	$V_{GS}(V)$	$I_D(mA)$	$V_{GS}(V)$	$I_D(mA)$
1	0	6.23	0	9.87
2	0.03	6.20	0.04	9.85
3	0.13	6.19	0.08	9.84
4	0.29	6.15	0.24	9.76
5	0.54	6.10	0.47	9.59
6	0.71	6.05	0.75	9.32
7	0.92	6.00	0.94	9.02
8	2.01	5.31	1.77	6.58
9	2.66	3.83	2.36	4.67
10	3.25	2.28	2.86	3.29
11	4.27	0.31	4.25	0.38
12	4.36	0.21	4.39	0.20
13	4.49	0.09	4.54	0.08
14	4.68	0.01	4.68	0.01
15	4.72	0	4.73	0

<https://alllabexperiments.com>

S.No	$V_{GS} = 1V$		$V_{GS} = 2V$	
	$V_{DS}(V)$	$I_D(mA)$	$V_{DS}(V)$	$I_D(mA)$
1	0.01	0.10	0.02	0.11
2	0.06	0.34	0.13	0.52
3	0.17	0.93	0.34	1.31
4	0.39	1.54	1.08	1.38
5	1.22	2.44	2.38	3.49
6	2.30	4.18	3.28	5.25
7	4.39	8.42	3.73	5.47
8	5.60	9.19	5.32	5.82
9	5.79	9.20	5.40	5.84
10	5.90	9.22	5.51	5.85
11				

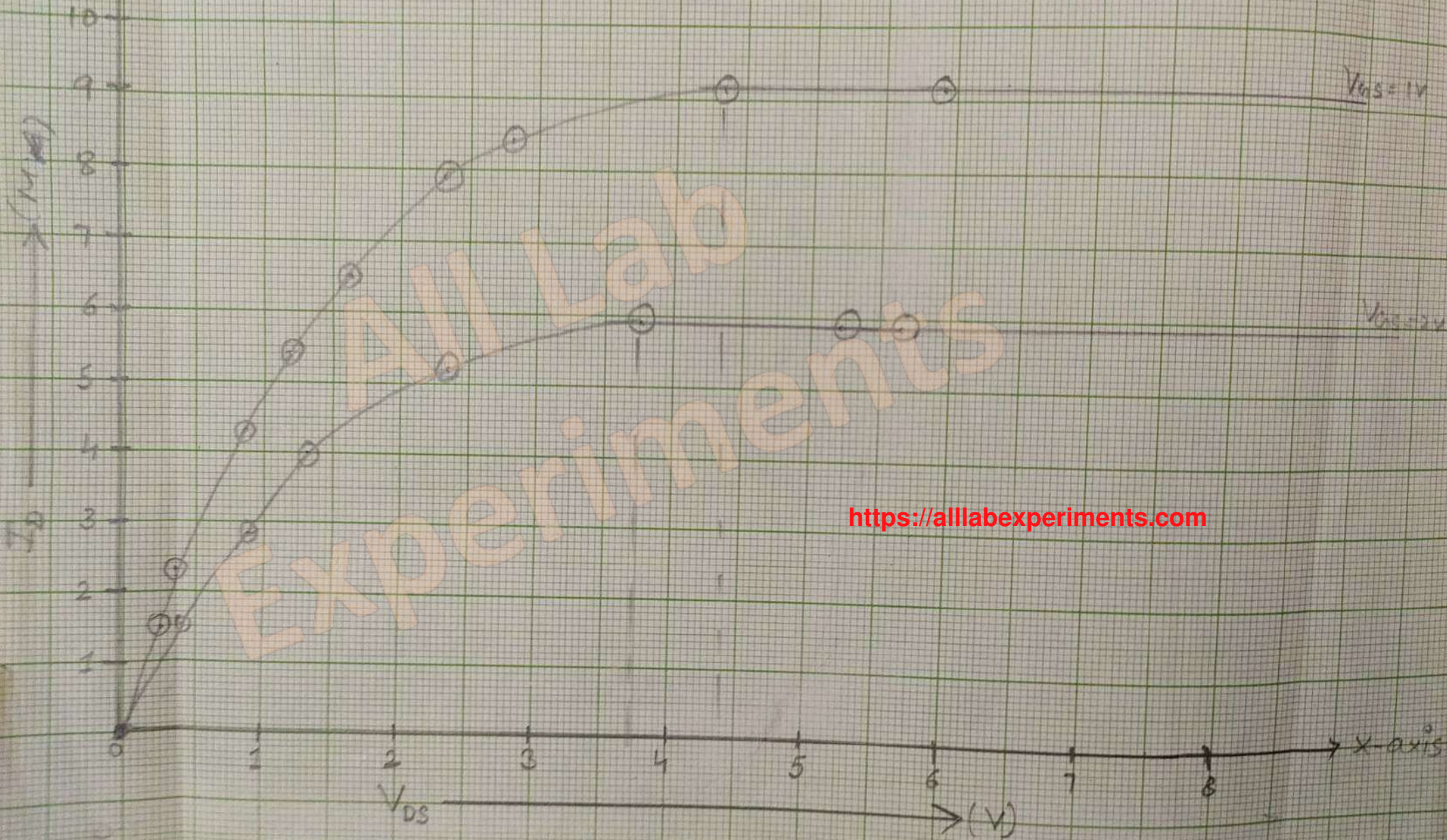Scale x-axis 1div = 0.05  
Y-axis 1div = 0.1



<https://alllabexperiments.com>

Current  $I_D$ .

⑧ Now change the value of  $V_{GS}$  and repeat step ⑦.

⑨ Now plot  $I_D$  versus  $V_G$  and trace the curve. The curve obtained is the transfer / input characteristic curve for Common Source FET.

<https://alllabexperiments.com>

RESULT - The I-V characteristic of Common Source FET has been studied and evaluated.