


AIM → Study of low pass and High pass RC filters.

APPARATUS → Resistance box, Capacitor box, Cathode ray Oscilloscope (CRO), audio frequency oscillator, connecting wires.

<https://alllabexperiments.com>

THEORY → Electronic circuits employ RC networks in a wide variety of circumstances. For example, if we use an RC combination to couple two stages of an amplifier. This circuit can be used as a low pass or High pass filter. The series combination of a resistance and a capacitor can differentiate or integrate a wave form. In addition, resistor and capacitor are inherent parts of all circuits and devices. Hence, it is desirable to have a thorough knowledge of characteristics of these circuits.

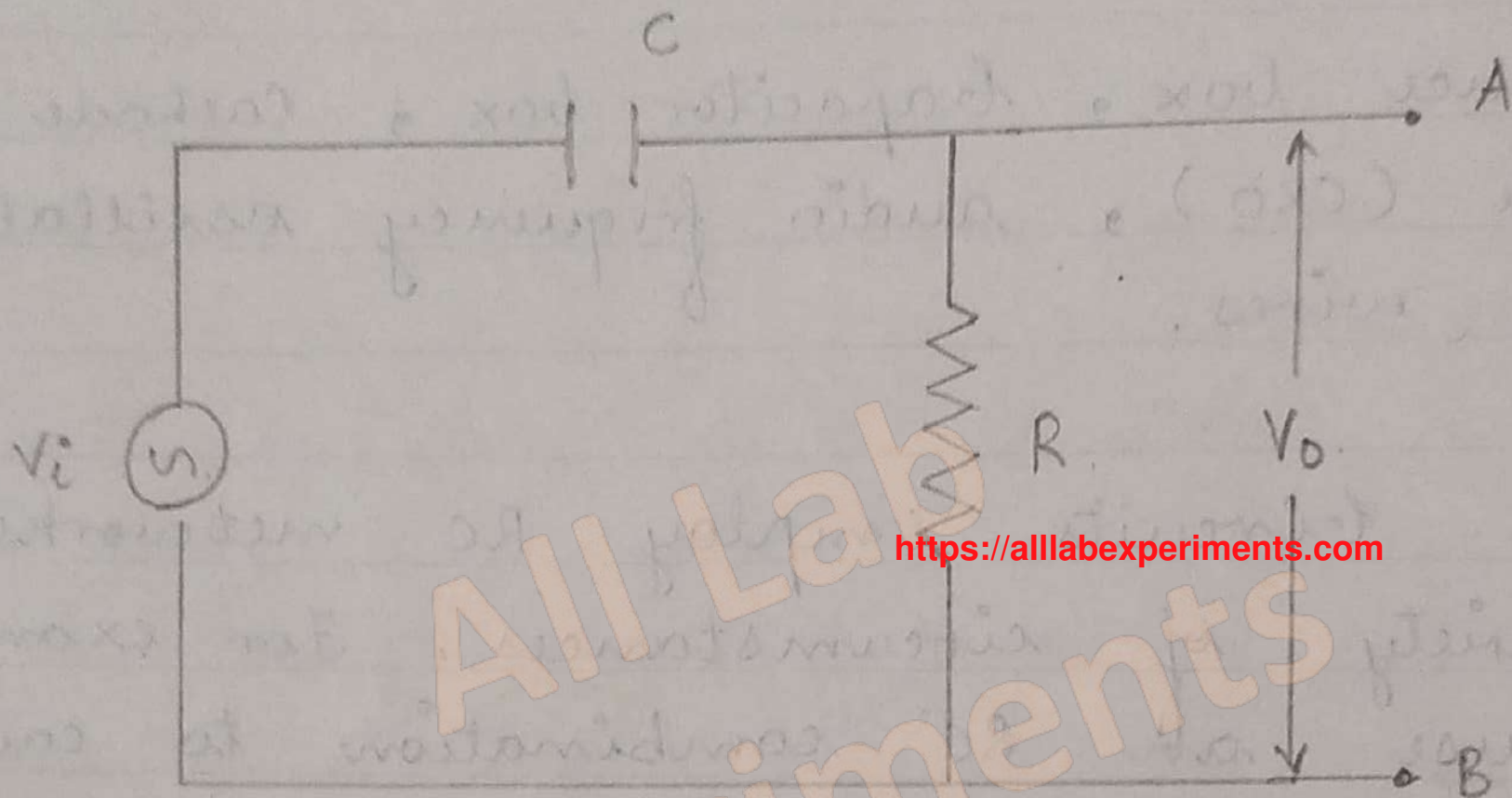HIGH PASS FILTER - The method of high pass filter is that in which output is taken across the resistance (R) as shown in the figure. It passes the high frequency and



<https://alllabexperiments.com>

<https://alllabexperiments.com>

HIGH-PASS FILTER

alternates the low frequency.

As we know,

$$V_{in} = I (X_c + R.) \quad \text{--- 1.}$$

where, V_{in} = input voltage

X_c = impedance across the capacitor.

Putting the value of $X_c = \frac{1}{j\omega C}$ in Eqⁿ 1.

$$V_{in} = I \left(\frac{1}{j\omega C} + R. \right)$$

$$= I \left(\frac{1 + jR\omega C.}{j\omega C.} \right)$$

$$\text{OR } I = \frac{V_{in} (j\omega C)}{1 + jR\omega C.}$$

<https://alllabexperiments.com>

Voltage drop across resistance is $V_o = IR.$

$$\therefore, V_o = \frac{V_{in} R(j\omega C)}{1 + jR\omega C.}$$

$$= \frac{V_{in} R j\omega C}{R j\omega C. \left(1 + \frac{1}{R j\omega C.} \right)} = \frac{V_{in}}{1 + \frac{1}{R j\omega C.}}$$

$$V_o = \frac{V_{in}}{1 + \frac{1}{j 2\pi f RC}}$$

$$= \frac{V_{in}}{1 - j f_o/f}$$

$$\theta = \tan^{-1} (f_o/f)$$

where f_o = cut off frequency.


CUT OFF FREQUENCY - It is that frequency at which the gain is full to $\frac{1}{\sqrt{2}}$ of its initial value.

$$\frac{V_o}{V_{in}} = \frac{1}{[1 + (f_o/f)^2]^{1/2}}$$

Special case,

1. If $f < f_o$, $f_o/f > 1$, so $\left| \frac{V_o}{V_{in}} \right| < 1$.

2. If $f = f_o$, $\left| \frac{V_o}{V_{in}} \right| = \frac{1}{\sqrt{2}}$

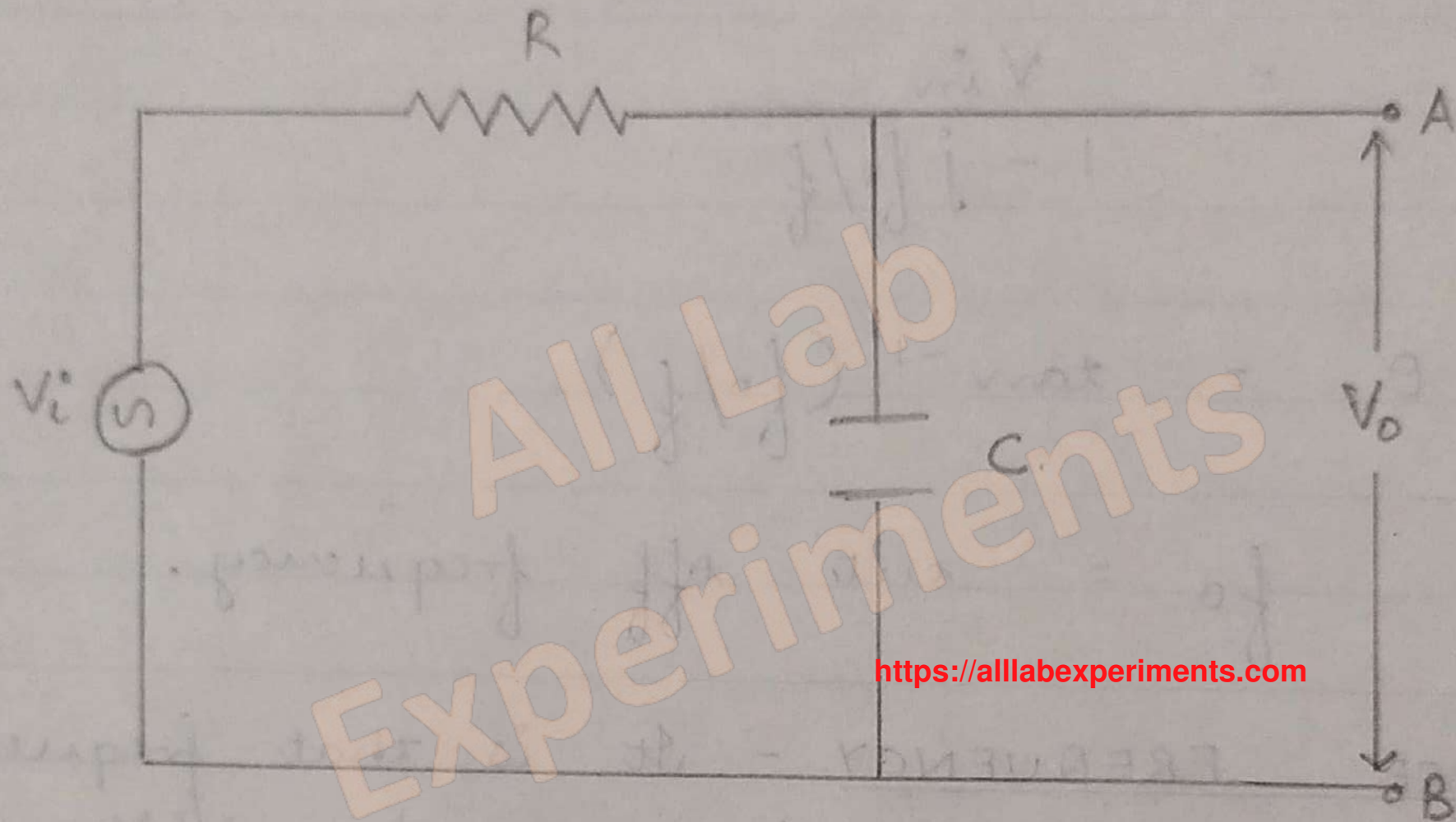

LOW PASS FILTER.

3. If $f > f_0$, $\left| \frac{V_o}{V_{in}} \right| \approx 1$

but off frequency of high pass filter is

$$f_0' = \frac{1}{2\pi RC} = 1500 \text{ Hz} \quad (\text{theoretically})$$

$$f_0'' \text{ (practically)} = 600 \text{ Hz} \quad (\text{practically})$$

LOW PASS FILTER. - The network acts as a low pass filter if output is taken across capacitor as shown in figure. It passes the low frequency and alternates the high frequency. As we know,

$$V_{in} = I (X_C + R)$$

$$= I \left(\frac{1}{j\omega C} + R \right) = I \left(\frac{1 + jR\omega C}{j\omega C} \right)$$

$$\therefore I = \frac{V_{in} j\omega C}{1 + jR\omega C}$$

<https://alllabexperiments.com>

Now voltage drop across capacitor is

$$V_o = I \times X_C$$

$$= \frac{V_{in} j\omega C}{1 + jR\omega C} \times \frac{1}{j\omega C} = \frac{V_{in}}{1 + j2\pi fRC}$$

$$f_0 = \frac{1}{2\pi RC} \quad (\text{cut off frequency})$$

$$\frac{V_o}{V_{in}} = \frac{1}{1 + i f/f_0} \quad \theta = \tan^{-1}\left(\frac{f}{f_0}\right)$$

$$\left| \frac{V_o}{V_{in}} \right| = \frac{1}{[1 + (f/f_0)^2]^{1/2}}$$

<https://alllabexperiments.com>

Special case,

1. If $f < f_0$, then f/f_0 being very less than one, so $V_o \approx V_{in}$.
2. If $f = f_0$, then $V_o = \frac{V_{in}}{\sqrt{2}}$, called the cut off frequency.
3. If $f > f_0$, then V_o decreases.

Cut off frequency of a low pass filter

$$f_0' = \frac{1}{2\pi RC} = 2000 \text{ Hz}$$

$$f_0 \text{ (practically)} = 1000 \text{ Hz}$$

PROCEDURE → 1. Design a high pass RC filter as shown in Fig 1. With some f_0 choose a resistance for such that its value is small in comparison to the input impedance. The capacitance is used as stated on the capacitor.

2. Keeping the input voltage V_i at a constant value measure the output voltage V_o on a CRO as a funcⁿ of frequency.

3. Evaluate the theoretical response and plot it on the V_o/V_i vs $\log f$ graph plotted.

4. Now design a low pass filter by interchanging the positions of resistance and capacitance and repeat the ~~above~~ process.

<https://alllabexperiments.com>

CALCULATIONS AND OBSERVATIONS →

HIGH PASS FILTER.

$$V_i = 1.5 \text{ V}$$

$$C = 0.1 \text{ } \mu\text{fd.}$$

$$f_0 = 1.5 \text{ KHz.}$$

From

$$f_0 = \frac{1}{2\pi RC.}$$


$$R = \frac{1}{2\pi f_0 C.}$$

HIGH PASS FILTER

SCALE:

X AXIS 1cm = 0.1
Y AXIS 1cm = 0.05

<https://alllabexperiments.com>

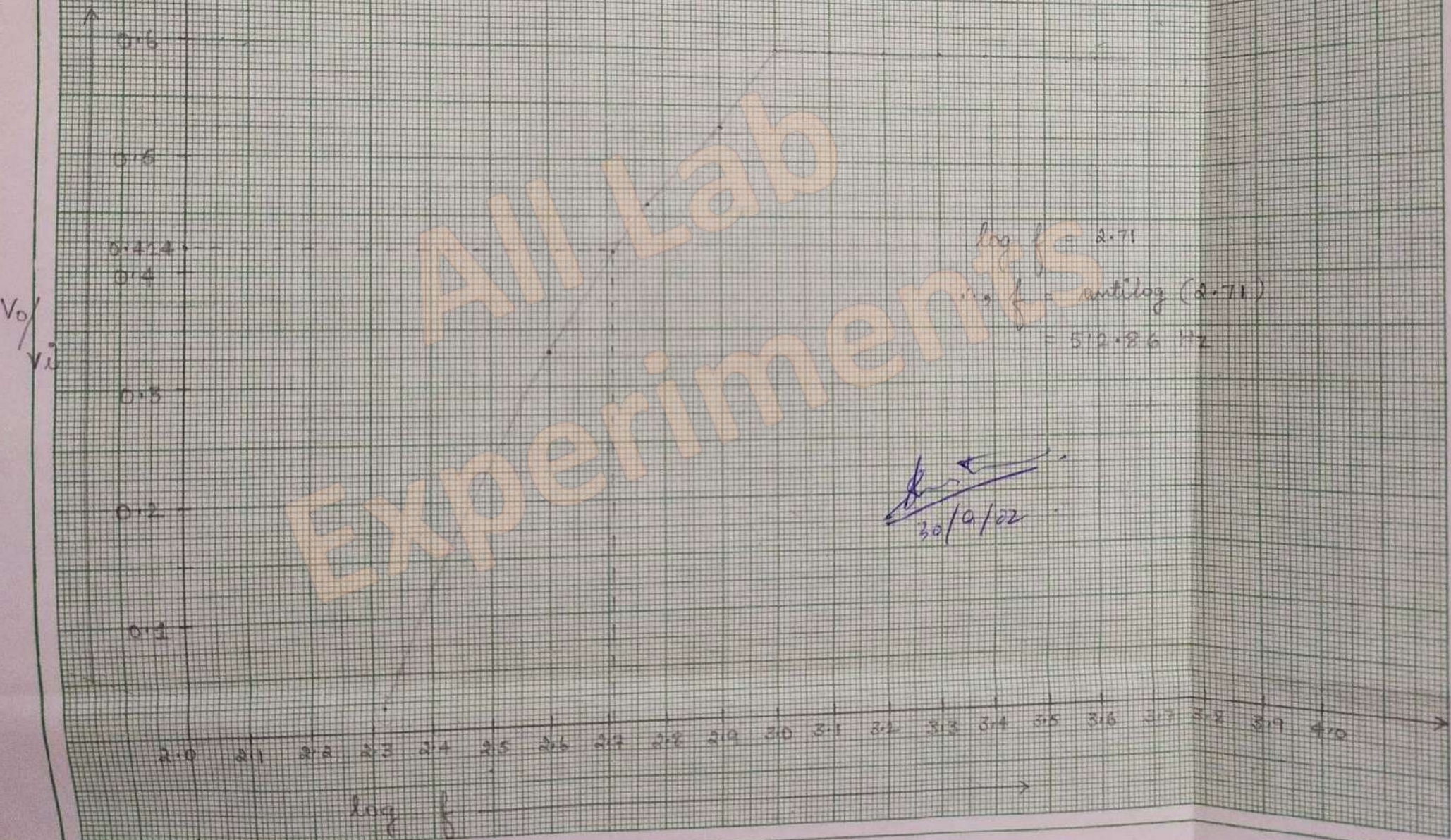

$$= \frac{1}{2 \times \frac{22}{7} \times 1500 \times 0.1 \times 10^{-6}} = 1060 \Omega$$

OBSERVATION TABLE

| Frequency f (Hz) | $\log f$ | Output Voltage V_o (V) | V_o/V_i |
|-----------------------|----------|-----------------------------|-----------|
| 210 | 2.32 | 0.03 | 0.02 |
| 400 | 2.60 | 0.50 | 0.33 |
| 600 | 2.77 | 0.70 | 0.46 |
| 800 | 2.9 | 0.80 | 0.53 |
| 1000 | 3.00 | 0.90 | 0.60 |
| 1200 | 3.07 | 0.90 | 0.60 |
| 1400 | 3.14 | 0.90 | 0.60 |
| 2000 | 3.30 | 0.90 | 0.60 |
| 1600 | 3.20 | 0.90 | 0.60 |
| 2500 | 3.39 | 0.90 | 0.60 |
| 4000 | 3.60 | 0.90 | 0.60 |

LOW PASS FILTER.

$$V_i = 2.8 \text{ V}$$

$$f_0 = 2 \text{ KHz}$$


$$C = 0.1 \mu\text{fd.}$$

LOW PASS FILTER.

Scale:
X-Axis = 1000 Hz
Y-Axis = 0.1

<https://alllabexperiments.com>

V_o/V_i

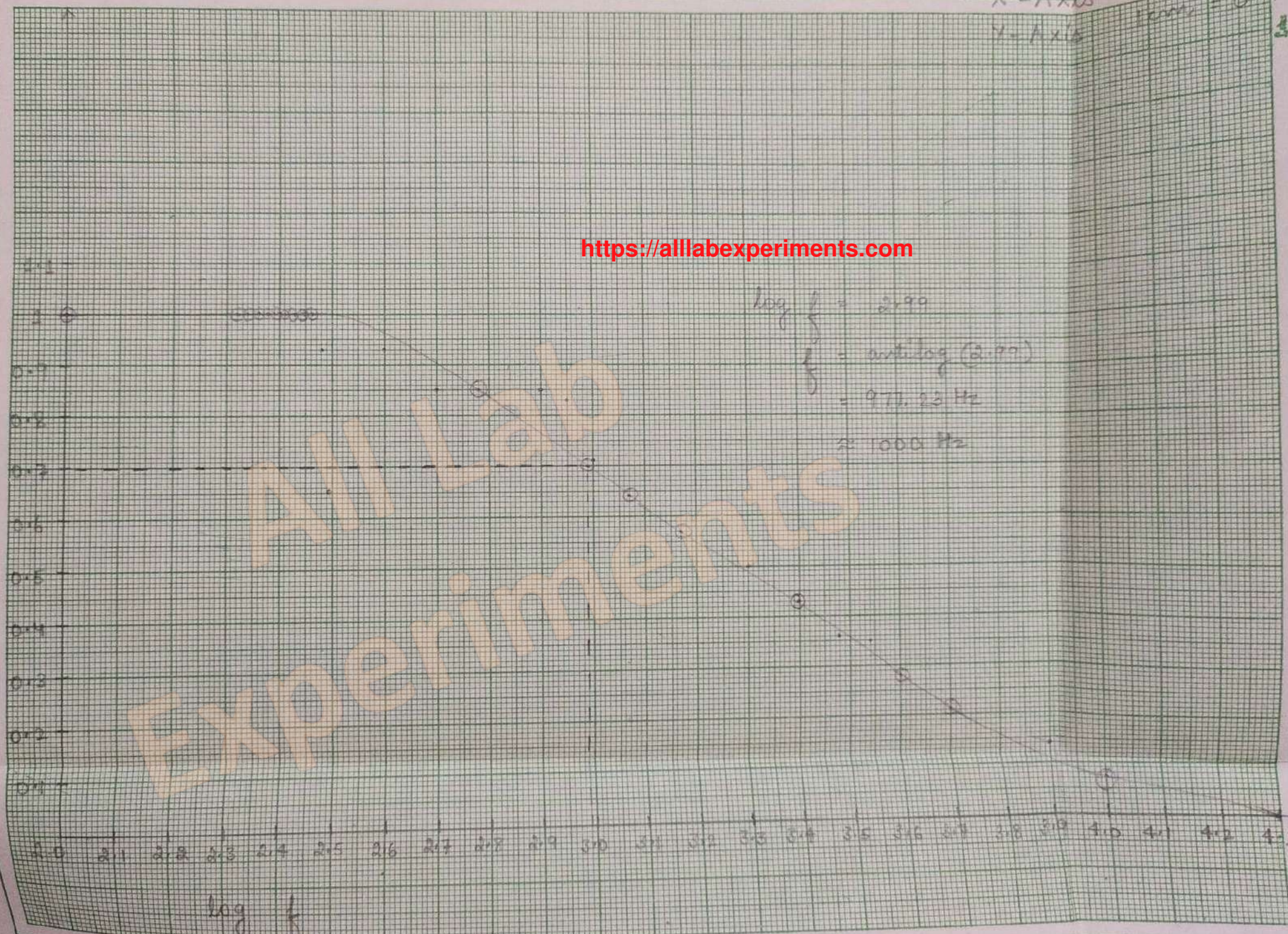

All Lab Experiments

$$\therefore R = \frac{1}{2 \times \frac{22}{7} \times 2 \times 10^3 \times 0.11 \times 10^{-6}} \approx 800 \Omega$$

OBSERVATION TABLE

<https://alllabexperiments.com>

| Frequency f (Hz) | $\log f$ | Output Voltage V_o (V) | V_o/V_i |
|-----------------------|----------|-----------------------------|-----------|
| 100 | 2 | 2.8 | 1 |
| 210 | 2.32 | 2.8 | 1 |
| 220 | 2.34 | 2.8 | 1 |
| 230 | 2.36 | 2.8 | 1 |
| 240 | 2.38 | 2.8 | 1 |
| 250 | 2.3979 | 2.8 | 1 |
| 260 | 2.41 | 2.8 | 1 |
| 270 | 2.43 | 2.8 | 1 |
| 280 | 2.447 | 2.8 | 1 |
| 290 | 2.46 | 2.8 | 1 |
| 300 | 2.477 | 2.6 | 0.9285 |
| 400 | 2.60 | 2.6 | 0.9285 |
| 500 | 2.6989 | 2.4 | 0.8571 |
| 600 | 2.778 | 2.4 | 0.8571 |
| 800 | 2.90 | 2.4 | 0.8571 |
| 900 | 2.954 | 2.2 | 0.7857 |
| 1000 | 3.000 | 2 | 0.7142 |

| | | | |
|-------|--------|-----|--------|
| 1200 | 3.079 | 1.8 | 0.6428 |
| 1500 | 3.156 | 1.6 | 0.5714 |
| 2000 | 3.30 | 1.4 | 0.50 |
| 2500 | 3.3979 | 1.2 | 0.4285 |
| 3000 | 3.477 | 1.0 | 0.3571 |
| 3500 | 3.54 | 1.0 | 0.3571 |
| 4000 | 3.60 | 0.8 | 0.2857 |
| 5000 | 3.69 | 0.6 | 0.2142 |
| 8000 | 3.90 | 0.4 | 0.1428 |
| 10 K. | 4 | 0.2 | 0.0714 |
| 20 K. | 4.30 | 0 | 0.00 |

RESULT → For a high pass filter <https://alllabexperiments.com>

$$f'_0 = 1500 \text{ Hz (theoretical)}$$

$$f'_0 = 600 \text{ Hz (practical)}$$

<https://alllabexperiments.com>

For a low pass filter

$$f'_0 = 2000 \text{ Hz (theoretical)}$$

$$f'_0 = 1000 \text{ Hz (practical)}$$

DISCUSSION →

We observe that practical value of the cut-off frequency are almost half of the theoretical value, in both the high pass and low pass RC filters. This may be due to some difference in the theoretical and practical value of the capacitor and the resistor. The other reason may be the difference in the theoretical and the actual frequency given by the audio oscillator which can lead to considerable differences in the value of cut-off frequency.

<https://alllabexperiments.com>

<https://alllabexperiments.com>