

Free Study Material from All Lab Experiments



**Electronics
for NET/Gate Physical Sciences
Logic Families # Oscillators**

**Support us by Donating
at the link "[DONATIONS](#)" given on the [Main Menu](#)**

**Even the smallest contribution of you
will Help us keep Running**

Logic Families

These are the technologies which are used to implement the logic function.

Logic Families

Saturated

Those logic families in which the devices enter into saturation region.

- RTL (Resistor Transistor Logic)
- DCTL (Direct Coupled Transistor Logic)
- I^2L (Integrated Injected Logic)
- DTL (Diode Transistor Logic)
- HTL (High threshold transistor Logic)
- TTL (Transistor-Transistor Logic)

Non-Saturated

Device does not enter in the saturation region.

- ECL [Emitter Coupled Logic]
- CMOS [Complementary metal oxide semiconductor technology]

* Characteristic parameters of Logic families :-


- ① Time propagation delay
- ② Power dissipation
- ③ figure of merit (FOM)
- x ④ fan in
- ⑤ fan out

⑥ Nois Margin

⑦ ~~High~~ Logic

① Time Propagation Delay :-

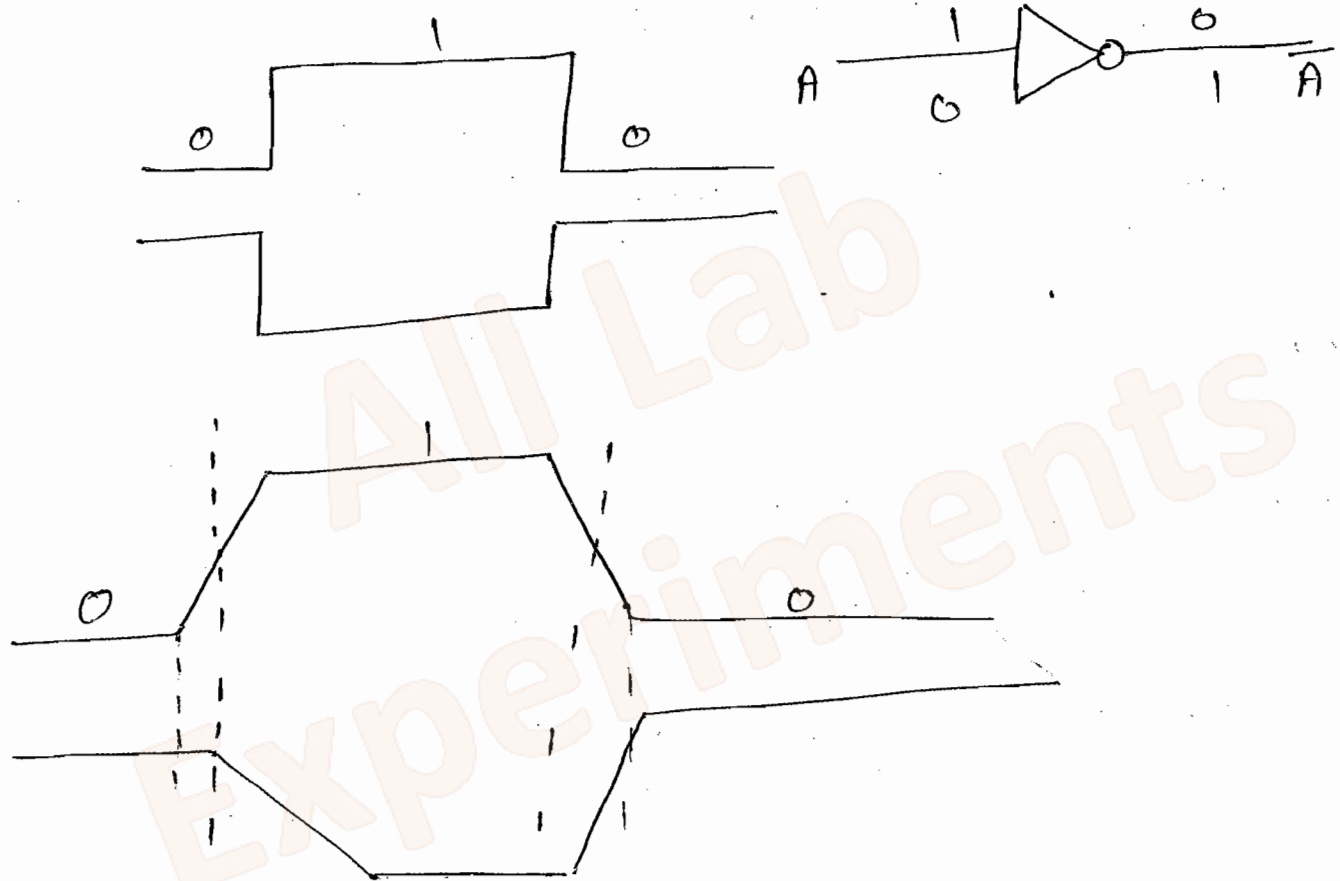It is the delay offered by per logic gate normally measured in nano second.



Delay is offered in the logic gate during the transition from high to low or low to high

Imp. \Rightarrow Fastest Logic family is ECL, HTL is slowest.

② Power Dissipation :-

Power expenditure inside

the logic gate to produce o/p.

CMOS has minimum power dissipation.

ECL has maximum power dissipation.

③ Figure of Merit (FOM) :-

Figure of Merit = Power dissipation \times power dissipation delay (n.s.)

Unit \rightarrow Pico Joule.

Figure of merit must be as low as possible.


I²L has best figure of merit

HTL has worst figure of merit.

④ fan in :-

Maximum no. of i/p's that can be applied to a logic gate.

⑤ fan Out :-

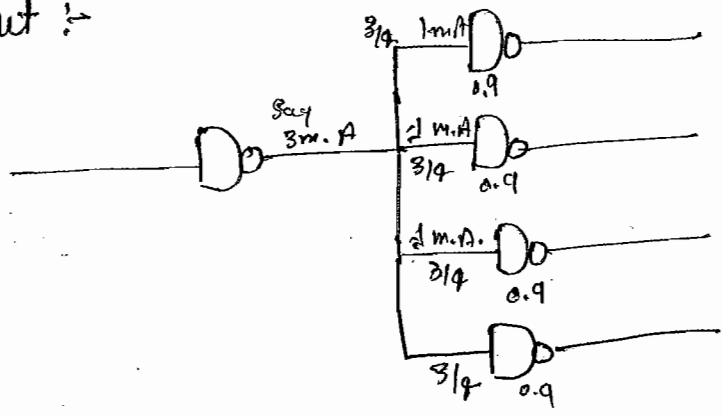


<https://alllabexperiments.com>

The output of one logic gate can be applied as input to the maximum no. of logic gate of same type is called as fan out.


CMOS : Maximum fan out

RTL : Minimum fan out.

⑥ Wired Logic :-

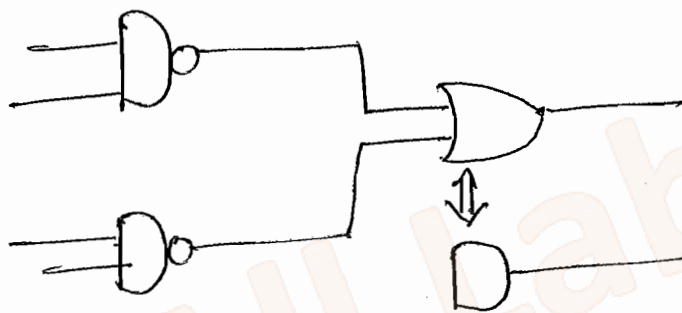

But

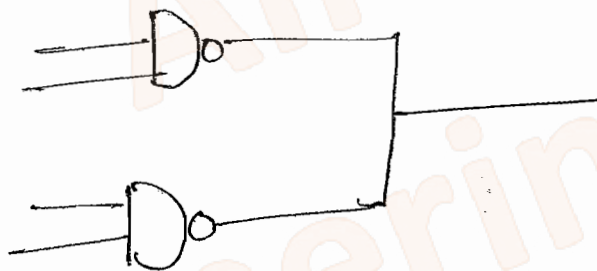

The output of two logic gate are joint at a point that point will behave as either OR-gate or AND-gate.

Only ECL behave as wired-OR rest all other logic behave as wired-AND.



⑦ Noise Margin :-

Maximum amount of noise added at the input so that it should not affect the output is called Noise Margin.



HTL \Rightarrow Best Noise Margin.

RTL \Rightarrow Worst Noise Margin



Q. Identify the logic gate.

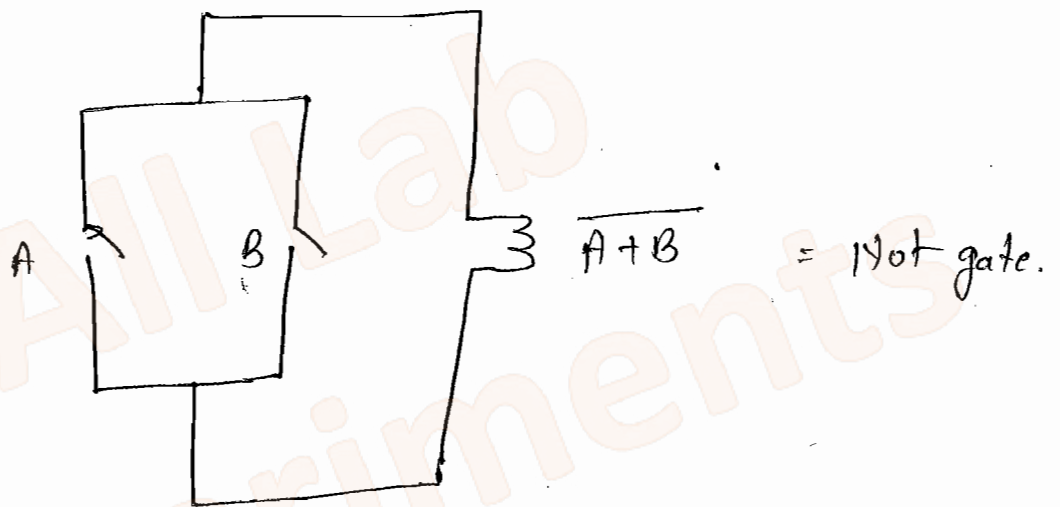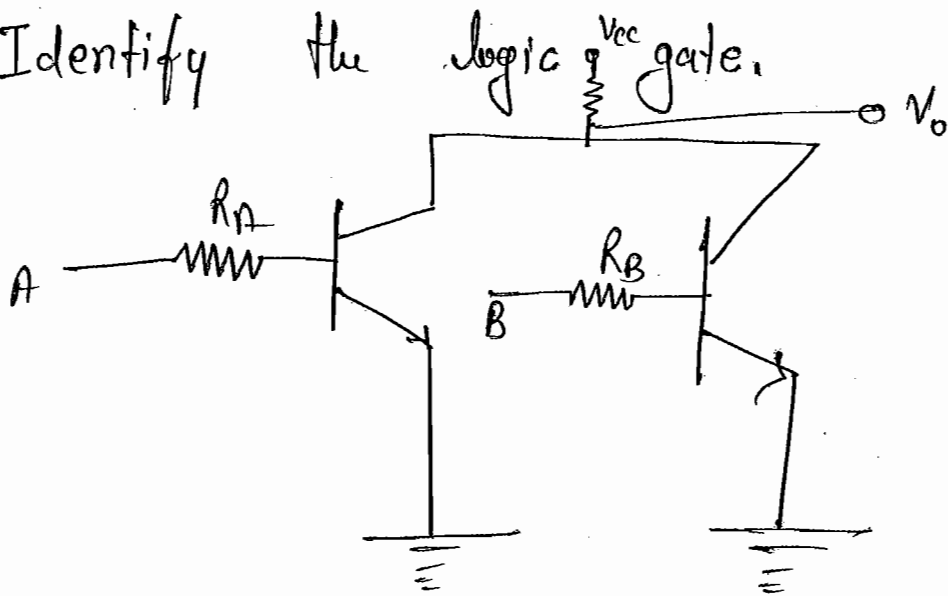



Q. Identify the logic gate.

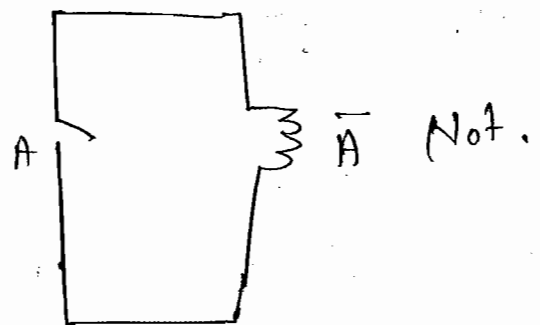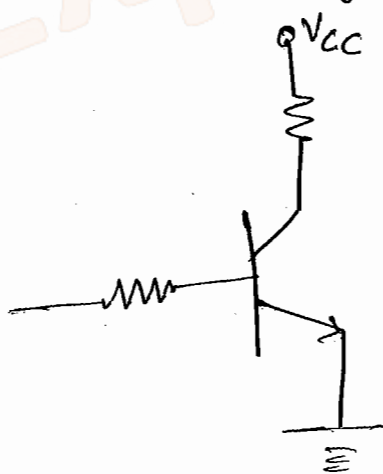

118

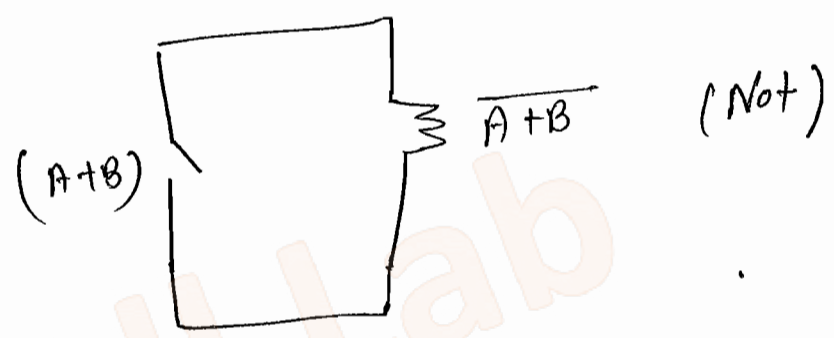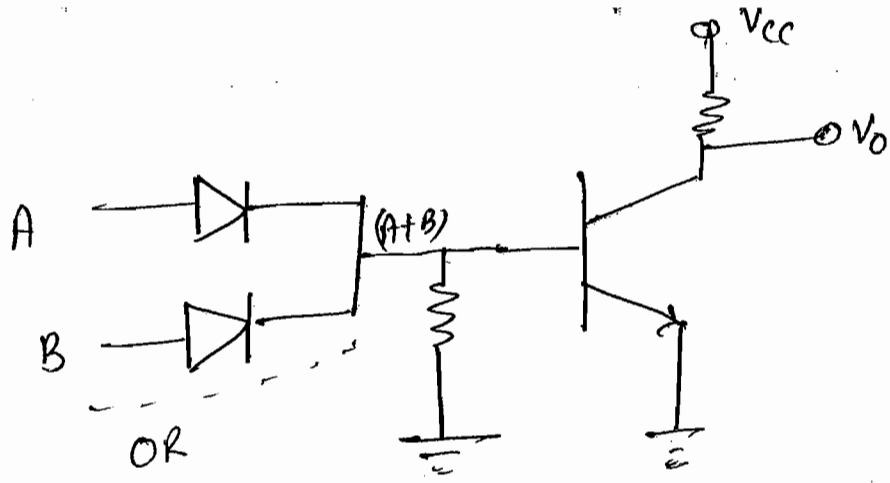

Q: Identify the logic gate

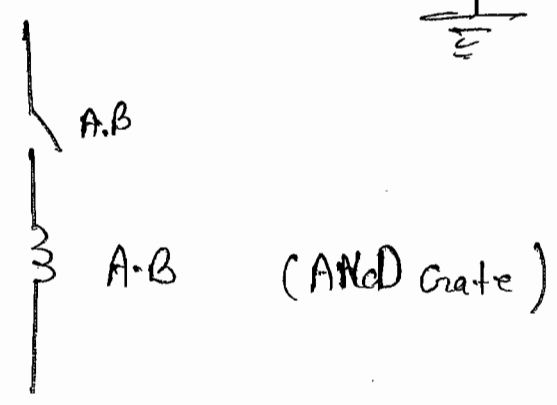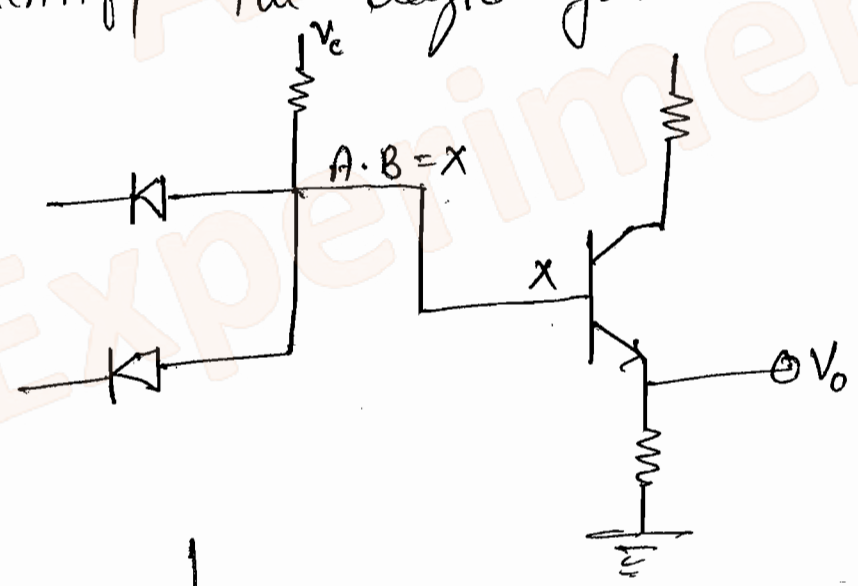


Parameters	RTL/DTL	I^2L	DTL	HTL	TTL	ECL	CM
Time propagation Delay				Slowest		fastest	
Power Dissipation						Max	Min
FOM							
fan out							
Noise Margin							
Wired Logic							
Basic gate							


All Lab Experiments

Oscillators

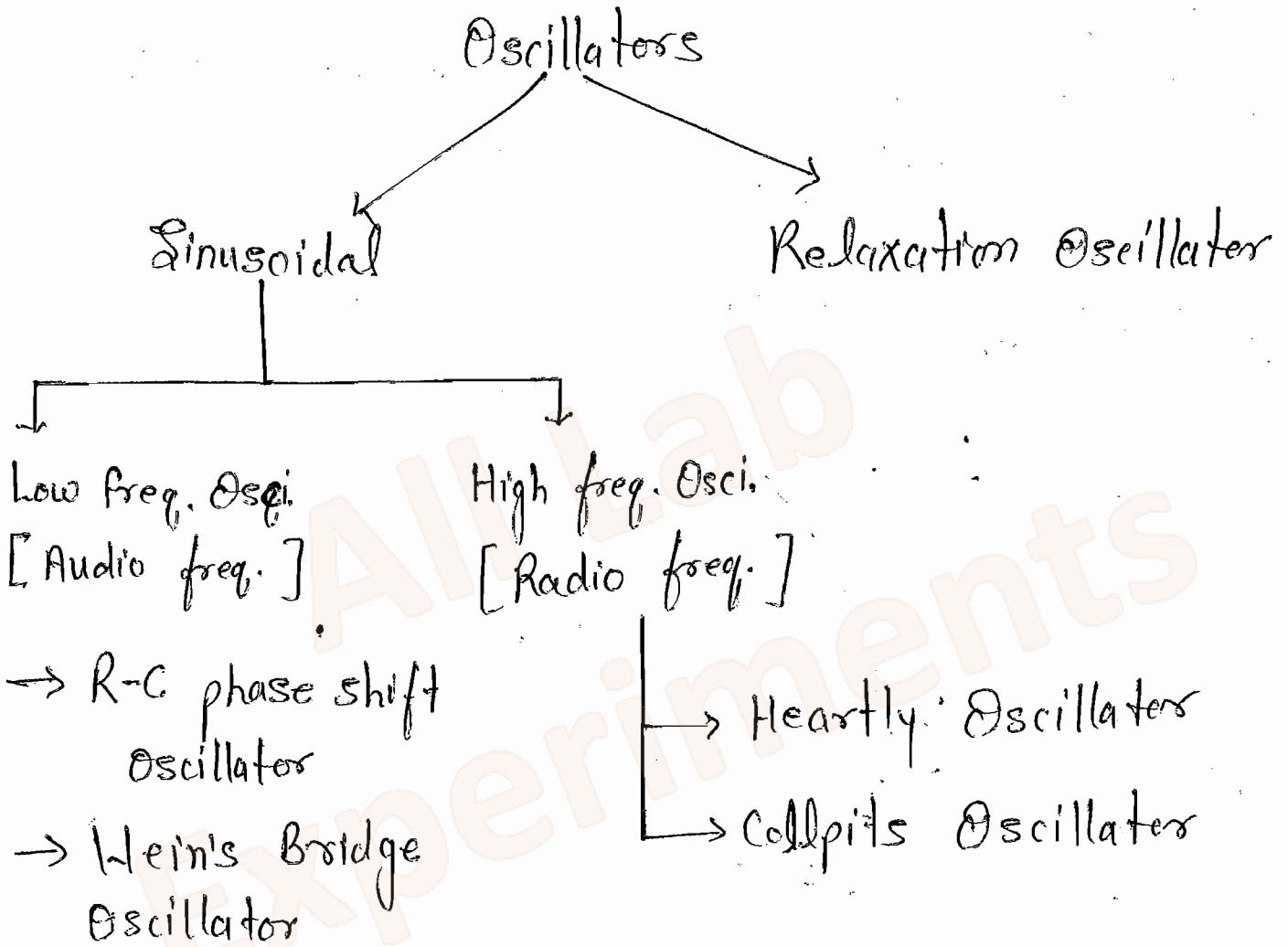Those circuit which produces sustained oscillations are called as oscillators.



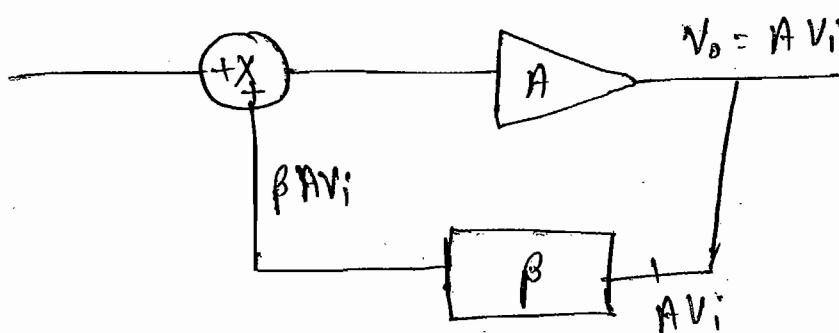In an oscillator always +ve feedback is used.



$$\therefore \frac{V_o}{V_{in}} = A$$


$$V_o = AV_i$$

Oscillator works without any external applied input.

Any disturbance (Noise) at the input may produce sustained oscillation.

Only if $|A\beta| = 1$ is ~~it~~ also called Barkhausen Criteria.

* R-C Phase Shift Oscillator :-

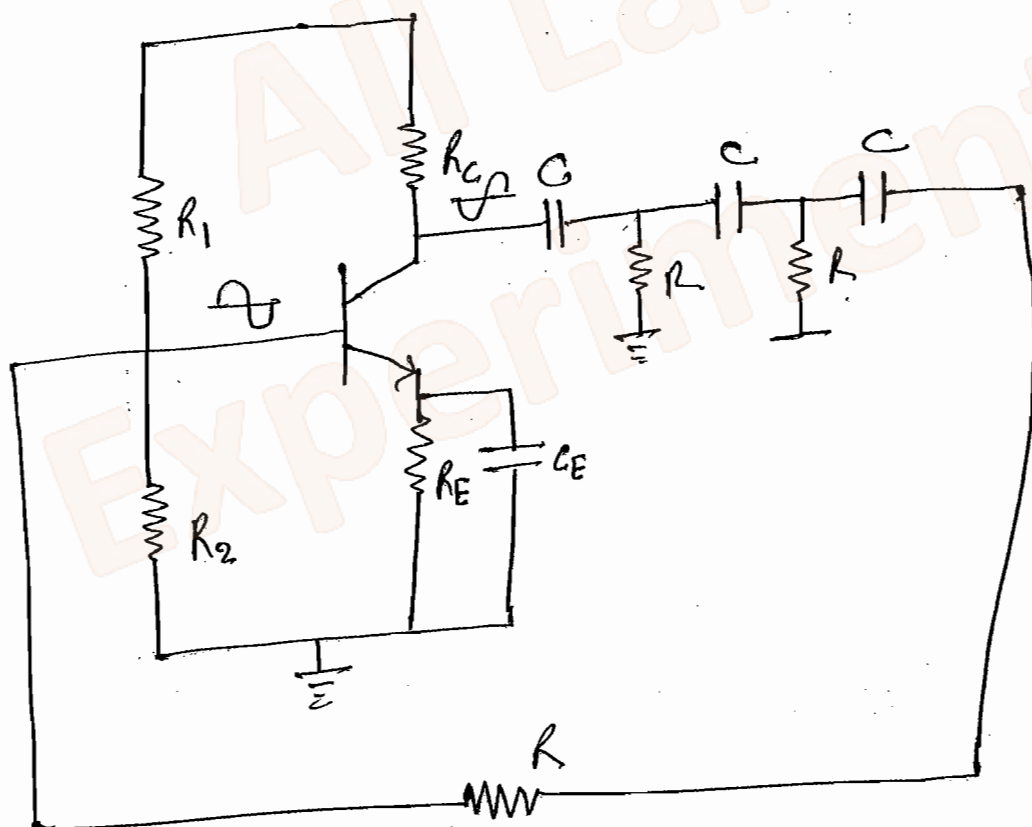

The output of the common emitter configuration produces the phase shift of 180° . The additional 3 R-C stages are used to provide a phase shift of additional 180° so that overall phase shift become $360^\circ (0^\circ)$.

So each R-C stage will provide 60° phase shift.


Expression for R-C phase shift:-

$$f_0 = \frac{1}{2\pi RC \sqrt{6 + 4\frac{R_c}{R}}}$$

When we can not use transistor then $R_c = 0$

$$f_0 = \frac{1}{2\pi RC \sqrt{6}}$$

* Wein's Bridge Oscillator:-

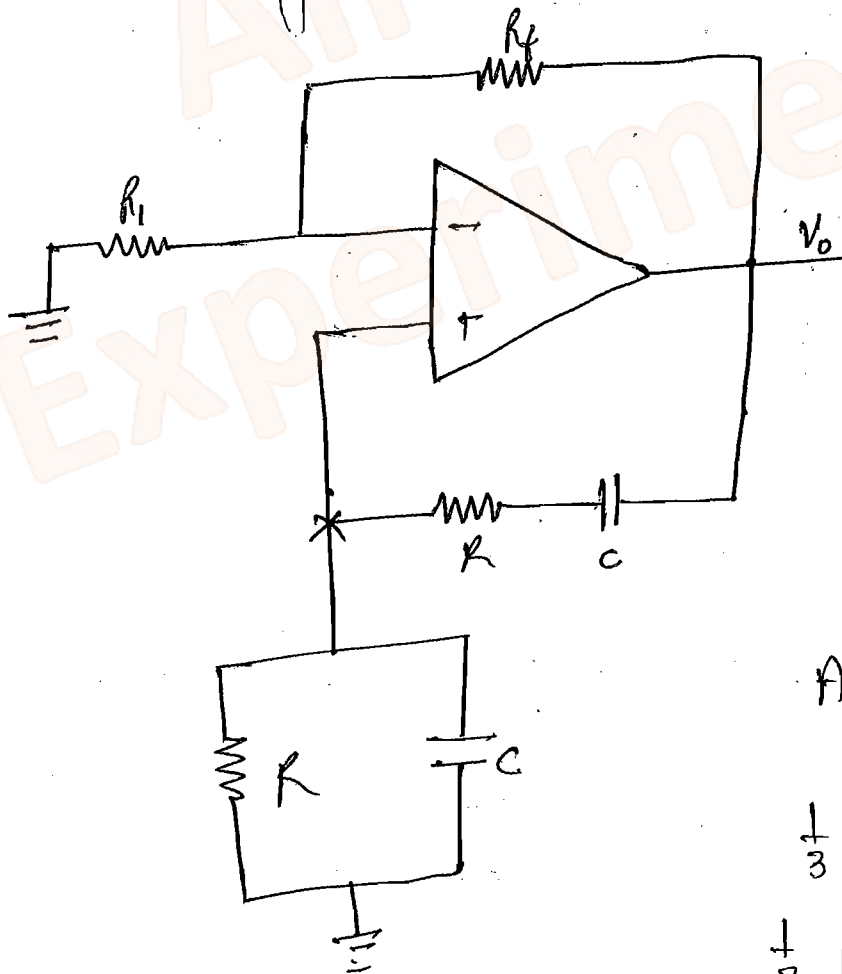

$$A = 1 + \frac{R_f}{R_1}$$


$$\frac{1}{3} A \geq 1$$

$$\frac{1}{3} \left(1 + \frac{R_f}{R_1} \right) \geq 1$$

$$\omega = \frac{1}{RC} \quad , \quad f = \frac{1}{2\pi RC}$$

$$Q_0 \quad \boxed{f_0 = \frac{1}{2\pi RC}}$$

B.A.
Q. 59

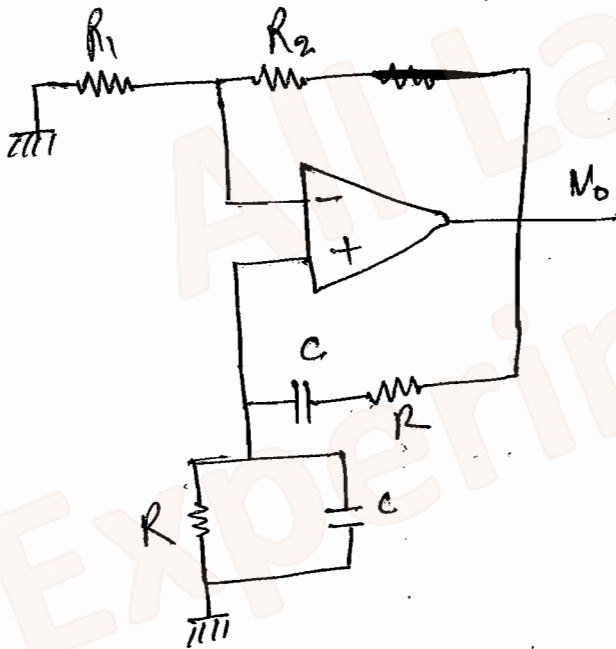

$$C = 0.01 \mu\text{F}$$

$$R_1 = 1 \text{ k}\Omega$$

$$f_0 = 300 \text{ Hz}$$

$$\therefore f_0 = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi \times 300 \times 0.01 \mu\text{F}}$$

$$= \frac{10^8}{300 \times 2\pi} = \frac{10^6}{6\pi}$$

$$= \underline{\underline{53 \text{ k}\Omega}} \quad 53 \times 10^3 \Omega$$

$$\boxed{R = 53 \text{ k}\Omega}$$

$$\frac{1}{3} A \geq 1$$

$$\frac{1}{3} \left(1 + \frac{R_2}{R_1} \right) = 1 \quad (\text{Worst Case})$$


$$1 + \frac{R_2}{R_1} = 3$$

$$\frac{R_2}{R_1} = 2$$

$$\frac{R_2}{12} = 2$$

$$\boxed{R_2 = 24} \quad \underline{\underline{\text{Ans}}}$$

* Hartley Oscillator :-

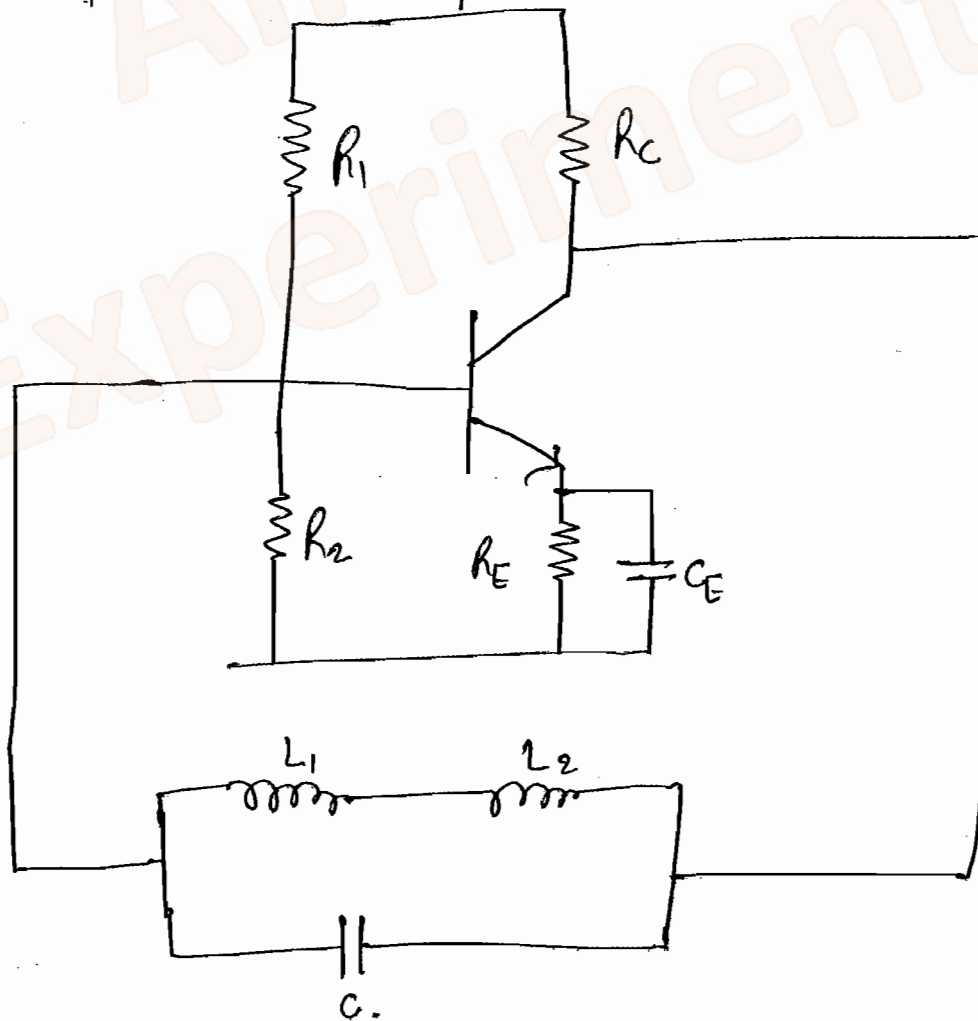

The output of G.E. Configuration provides a phase shift of 180° additional phase shift in tank circuit is used so that it can provide a phase shift of 180° . To provide sustained oscillation.

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$


$$\omega = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{L_{eq} C_{eq}}}$$

$$f_0 = \frac{1}{2\pi\sqrt{(L_1 + L_2)C}}$$

Collpits Oscillator :-

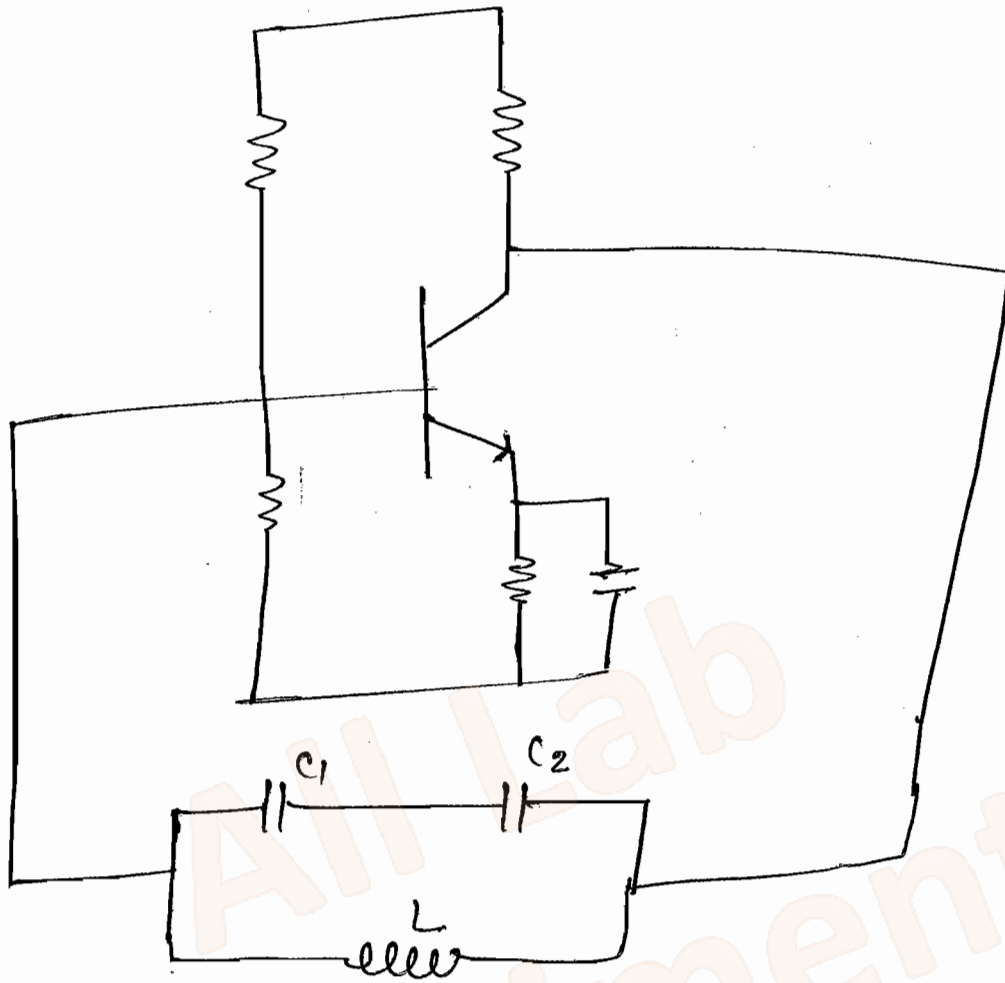

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{L} \cdot \frac{1}{C}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{L_{eq}} \cdot \frac{1}{C_{eq}}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\left(\frac{1}{C_1} + \frac{1}{C_2}\right) \frac{1}{L}}$$

RC phase Shift

$$f_0 = \frac{1}{2\pi RC \sqrt{1 + 4 \frac{R_c}{R}}}$$

Hein's Bridge

$$f_0 = \frac{1}{2\pi RC}$$

Hearstly

$$f_0 = \frac{1}{2\pi \sqrt{(L_1 + L_2)C}}$$


Collpits

$$f_0 = \frac{1}{2\pi \sqrt{\left(\frac{1}{C_1} + \frac{1}{C_2}\right) L}}$$

Net-2013

Q. 85

<https://alllabexperiments.com>

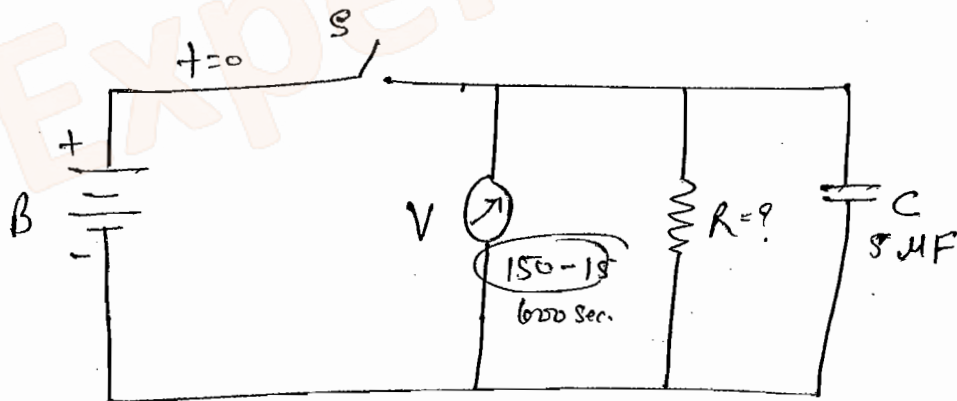

$$\omega = \frac{1}{RC}$$


$$T = \frac{1}{\omega} = RC \quad \left\{ \text{Time } \propto \frac{1}{\text{cut-off freq.}} \right\}$$

$$T = RC$$

$$R = \frac{1000}{5 \mu\text{F}} = 2 \times 10^5 \approx 10^5 \Omega$$

B-11
Q.77

Solⁿ

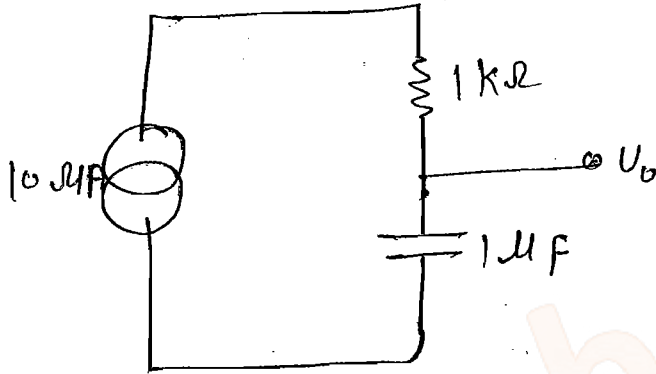

$$T = RC$$

$$= 1 \text{ k}\Omega \times 1 \mu\text{F} = 1 \times 10^{-3} = \text{1 millisecond.}$$

A

B.A.

Q.85

Second Method

$$V = 15$$

$$T = 1000$$

$$C = 5 \mu\text{F}$$

$$R = ?$$

$$Q = CV$$

$$Q = 5 \mu\text{F} \times 15$$

$$= 75 \mu\text{C}$$

$$Q = it$$

$$i = \frac{Q}{t} = \frac{75 \mu\text{C}}{1000}$$

$$I = 75 \text{ m.A.}$$

$$R = \frac{15}{75} \times 10^9 = 2 \times 10^8 \Omega$$

* Consenses Theorem :-

$$Y = AB + BC + \bar{A}C$$

$$Y = AB + BC(A + \bar{A}) + \bar{A}C$$

$$= AB + AB C + \bar{A} B C + \bar{A} C$$

$$= AB [1 + C] + \bar{A} C [B + 1]$$

$$Y = AB + \bar{A} C$$

Steps:-

- ① Total no. of variable in use = 3
- ② Every variable must be repeated twice.
- ③ Select to the term which one is the compliment of other which is ans.

Q. Find the minimise expression $Y = AB + \bar{B}C + AC$

Solⁿ

$$Y = AB + \bar{B}C$$

Q.

$$Y = AB + \bar{B}C + AC$$

Solⁿ

$$Y = \bar{B}C + AC$$

Q.

$$Y = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C}$$

Solⁿ

$$Y = \bar{A}\bar{B} + \bar{A}\bar{C}$$

Q. $Y = AB + \bar{A}C + B\bar{C}$

Soln

$$Y = AB + \bar{A}C$$

Q. $Y = (A+B)(B+C)(\bar{A}+C)$

Soln

$$Y = (\bar{A}+B)(\bar{A}+C)$$

Q. $Y = (\bar{x} + \bar{y})(\bar{y} + \bar{z})(x + \bar{z})$


Soln

$$Y = (\bar{x} + \bar{y})(x + \bar{z})$$


Ans

Q. D.V. The current gain in the transistor $\beta = 100$ the value of collector current I_c is?

(a)

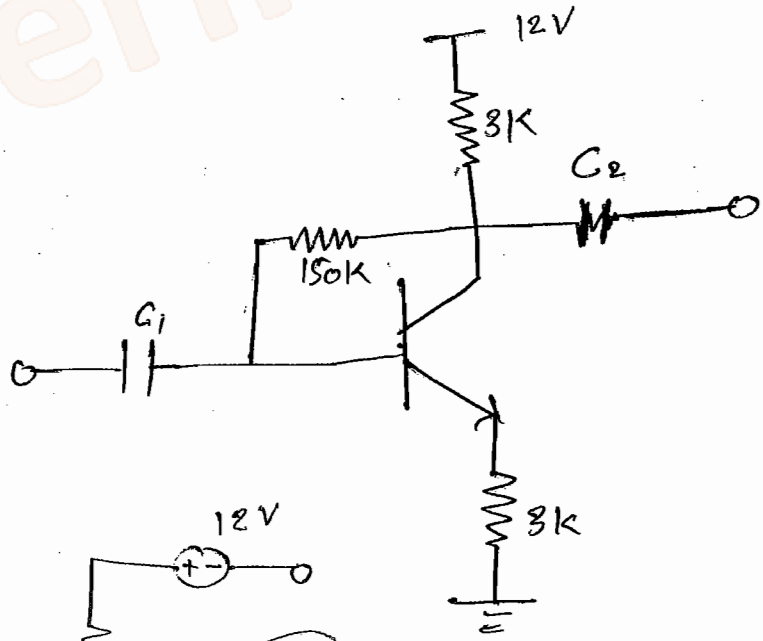

Soln

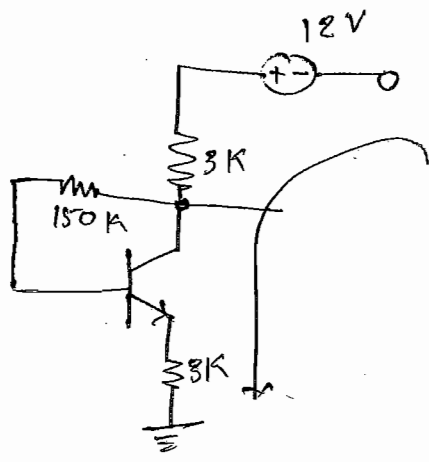

$$-12 + (I_E + I_B) 3k + I_B \times 150k + V_{BE} + I_E \times 3k = 0$$

$$(I_E + I_B) 3k + I_B 150k + (I_B + I_C) 3k = 11.3$$

$$I_C 3k + I_B 3k + I_B 150k + I_B 3k + I_C 3k = 11.3$$

$$I_C 6k + I_B 156k = 11.3$$

$$\beta I_B 6k + I_B 156k = 11.3$$

$$100 \times 6k I_B + 156k I_B = 11.3$$

$$756 I_B = 11.3$$

$$I_B = \frac{11.3}{756} = 0.014 \text{ m.A.}$$

$$I_C = \beta I_B$$

$$= 100 \times 0.014 \text{ m.A.}$$

$$= 1.4 \text{ m.A.} \quad \underline{\underline{Ans}}$$

In order to measure a maximum of 1V with a resolution of 1 millivolt using n-bit analog to digital converter determine n-bit?

Solⁿ

$$\text{resolution} = 1 \text{ m.V}$$

$$V_r = 1V$$

$$\text{reso} = \frac{V_r}{2^n - 1}$$

$$\Rightarrow 1 \text{ m.V.} = \frac{1}{2^n - 1}$$

$$2^n - 1 = \frac{1}{1 \text{ m.V.}}$$

$$2^{11} - 1 = 1000$$

$$2^n = 1001$$

$$2^n \approx 2^{10}$$

$$\boxed{n = 10}$$

Q. A low pass filter formed by simple R-C circuit at the cut-off angular frequency. the voltage gain and the phase of output voltage relative to input voltage respectively are -


(a) $0.71 \angle +95^\circ$

(b) $0.71, -95^\circ$

(c) $0.5 \angle -90$

(d) $0.5 \angle +90^\circ$

Solⁿ

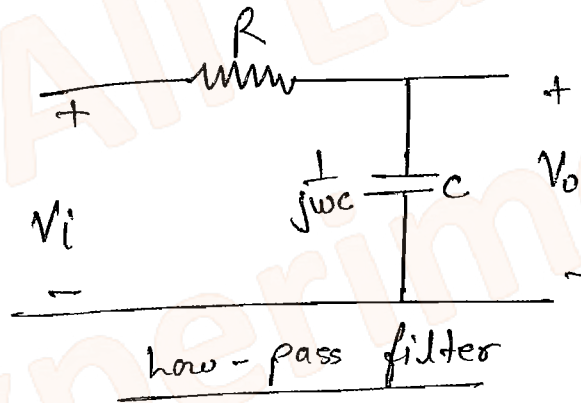

$$V_o = \frac{V_i \times \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$\frac{V_o}{V_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$
$$= \frac{1}{\sqrt{1 + \left(\frac{\omega}{\frac{1}{RC}}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

$$\omega = \omega_c$$

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$


$$\frac{V_o}{V_i} = \frac{1}{1+j\omega RC}$$

$$\angle \frac{V_o}{V_i} = -\tan^{-1}(\omega RC) = -\tan^{-1}\left(\frac{\omega}{\frac{1}{RC}}\right)$$

$$= -\tan^{-1}\left(\frac{\omega}{\omega_c}\right) = -\tan^{-1}\left(\frac{\omega}{\omega}\right)$$

$$= -\tan^{-1}(1) = -\tan^{-1}(\tan 45^\circ)$$

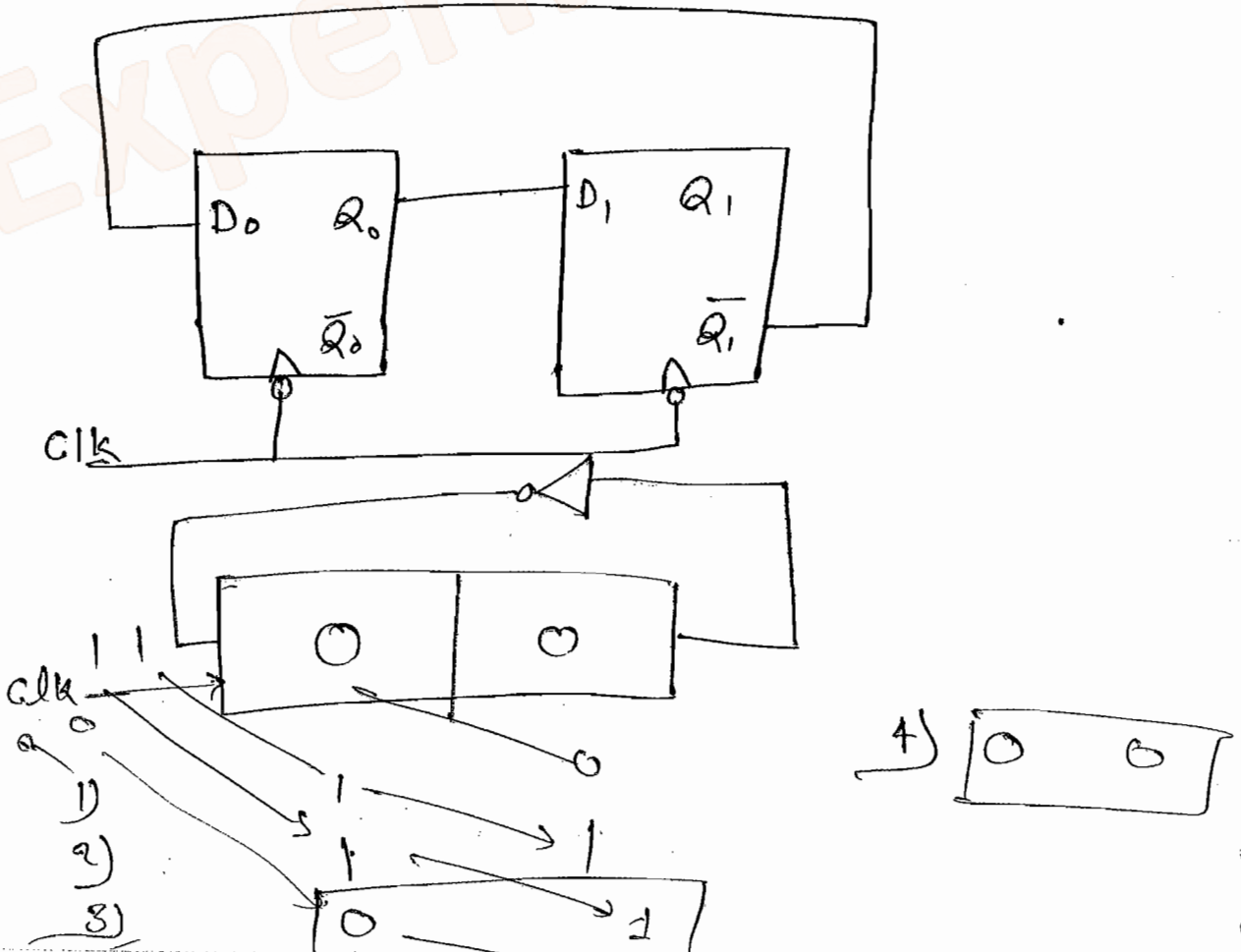
$$= \underline{\underline{-90^\circ}} \quad \underline{\underline{\text{Ans}}}$$



~~335~~ OP.


$$4 \overline{) 335} \\ \underline{37} \\ 15 \\ \underline{12} \\ 3 \rightarrow$$

2

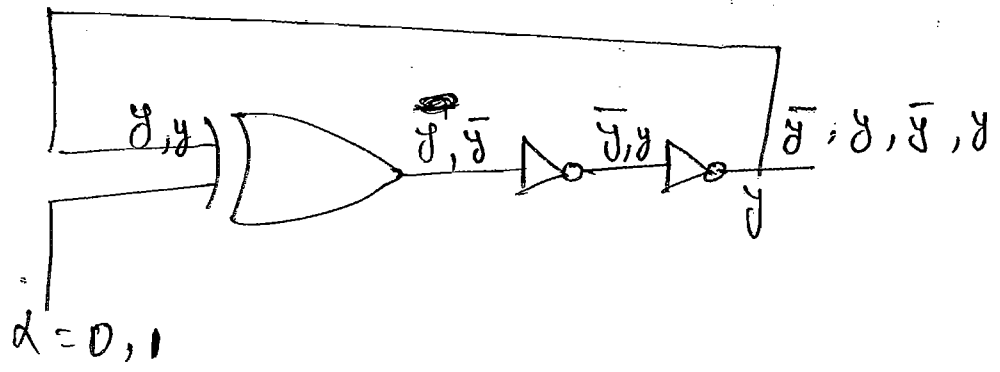

So $X=1$

3

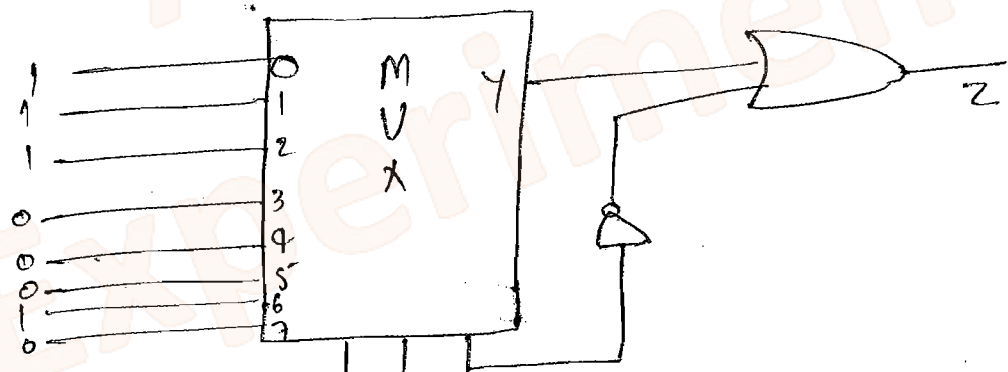

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


$$\bar{A}\bar{B}\bar{C} \cdot 1 + \bar{A}\bar{B}C \cdot 1 + \bar{A}B\bar{C} \cdot 1 + AB\bar{C} \cdot 1 = Z$$

$$Z = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + AB\bar{C} + \bar{C}$$

$$= \bar{A}\bar{B} + \bar{C} [1 + AB + \bar{A}B]$$

$$Z = \bar{A}\bar{B} + \bar{C}$$

4

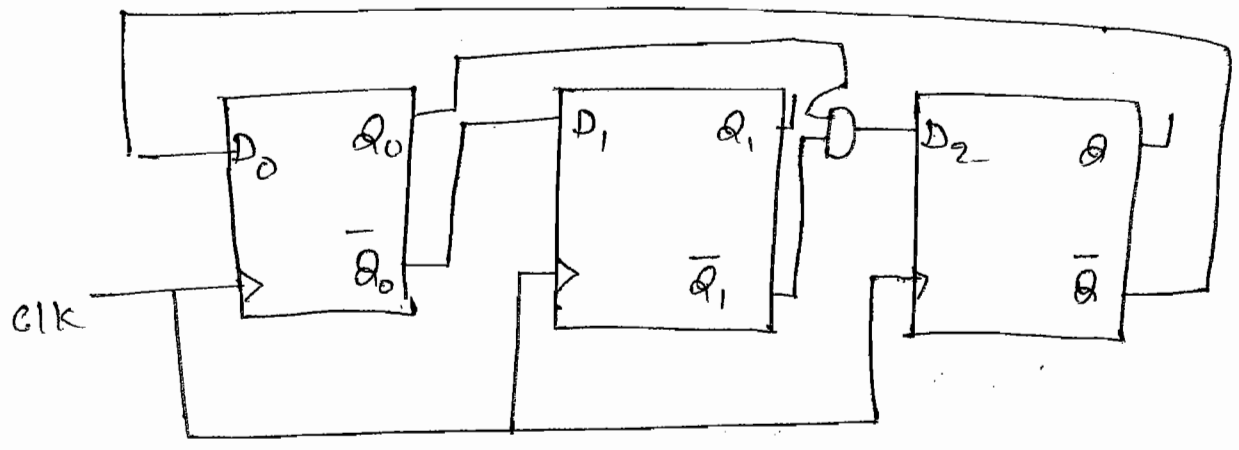

$$D_1 = \bar{Q}_0$$

$$D_0 = \bar{Q}_2$$


$$D_2 = \bar{Q}_0 \bar{Q}_1$$

<https://alllabexperiments.com>

	D_0	D_1	D_2	Q_0	Q_1	Q_2
X	1	1	0	0	0	0
1)	1	0	0	1	1	0
2)	1	0	1	1	0	0
3)	0	0	1	1	0	1
4)	0	1	0	0	0	1
5)	1	1	0	0	1	0
	1	1	0	1	1	0

mod - 5

5

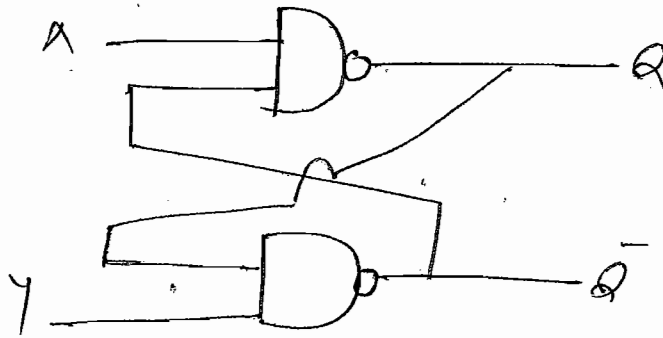


$X=0, Y=0$ invalid (a)

6

	AB	00	01	11	10
C	1	1	1	X	0
0	0	0	X	0	

$$Y = C\bar{A}$$


Q. Identify the flip-flop.

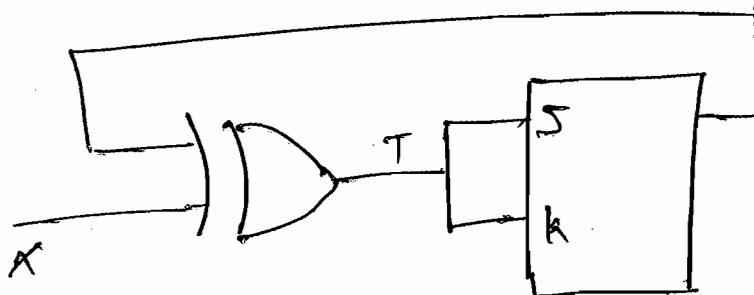



$$T = a_1 \oplus Q$$

So $a_1 = D$

Q. Identify

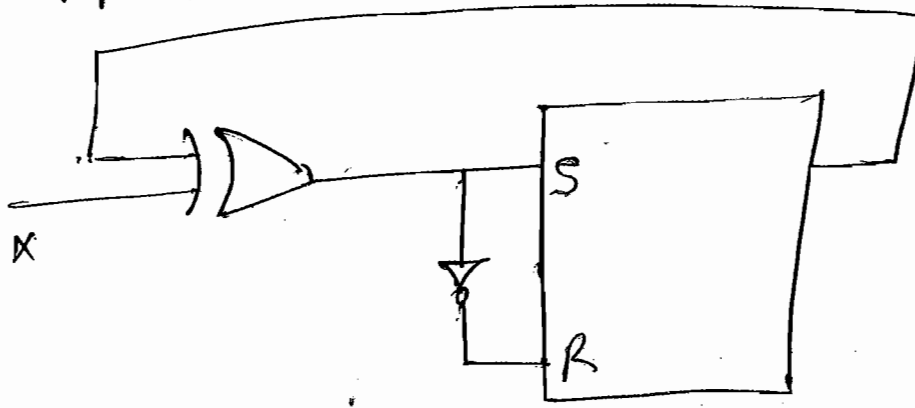

T-flip-flop.

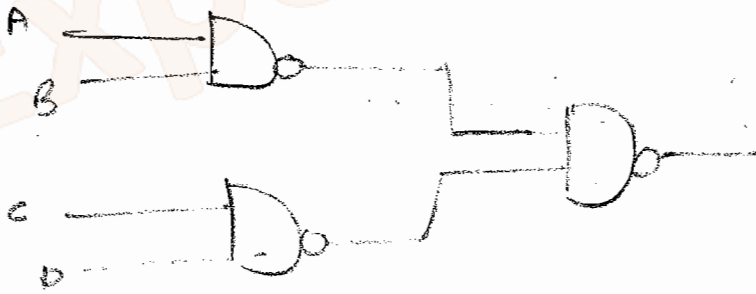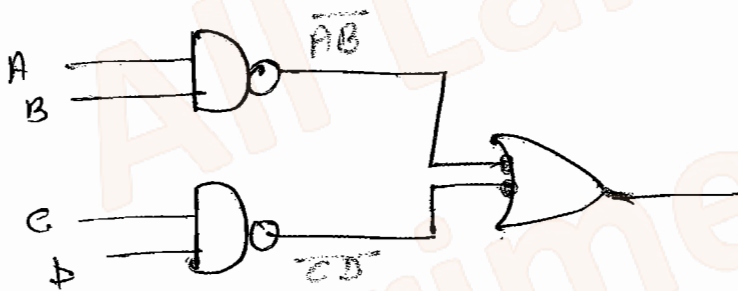

∴ min^m no. of nand gate required = 3.