

Free Study Material from All Lab Experiments



**Electronics
for NET/Gate Physical Sciences
Flip-Flops # Rectifiers**

**Support us by Donating
at the link "[DONATIONS](#)" given on the [Main Menu](#)**

**Even the smallest contribution of you
will Help us keep Running**

~~* fix~~

* Flip-Flop Conversion :-

Steps -

- (i) Identify the flip-flop which is required.
 - (ii) Draw the characteristic table.
 - (iii) Develop the excitation table for the ~~required~~ ^{given} flip-flop. Minimise by k-map.
 - (iv) Implement by logic gates.
- (i) Convert JK to T-flip-flop :-

T	Q_n	Q_{n+1}	J	K
0	0	0	0	X
0	1	1	X	0
1	0	1	1	X
1	1	0	X	1

Q_n	Q_{n+1}	S	R
0	0	0	X
0	1	1	0
1	0	0	1
1	1	X	0


T	Q_n	0	1
0	0	0	X
1	0	1	X

$J = T$

T	Q_n	0	1
0	0	X	0
1	0	X	1

$K = T$

J	K
0	X
1	X
X	1
X	0

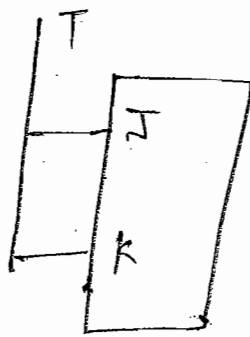

T-flip-flop

* Convert JK to \oplus flip-flop :-


D	Q_n	Q_{n+1}	JK
0	0	0	0 X
0	1	0	X 1
1	0	1	1 X
1	1	1	X 0

Q_n	0	1
0	0	X
1	1	X

$J = D$

Q_n	0	1
0	X	1
1	X	0

$K = \bar{D}$

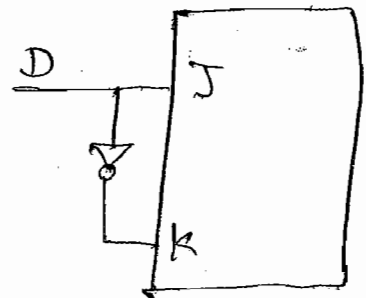

* Convert D to T flip-flop :-

T	Q_n	Q_{n+1}	D ($= Q_{n+1}$)
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

T \ Q_n	0	1
0	0	1
1	1	0

$$D = \bar{T} Q_n + T \bar{Q}_n$$

$$D = T \oplus Q_n$$

or

$$T = D \oplus Q_n$$

* Point To be remember :-

$$JK \longrightarrow T$$

$$J = T$$

$$K = T$$

$$JK \longrightarrow D$$

$$J = D$$

$$K = \overline{D}$$

$$SR \longrightarrow D$$

$$S = D$$

$$R = \overline{D}$$

$$D \longrightarrow T$$

$$D = T \oplus Q_n$$

$$T \longrightarrow D$$



$$T = D \oplus Q_n$$

All Lab Experiments

* Steps for identification

- ① Draw the circuit diagram by using ordinary gate
- ② Substitute bubble in front of AND gate and input of OR gate so that bubble is balanced.
- ③ Replace every gate by Nand gate, it gives min^m no. of nand gate.


Ex -

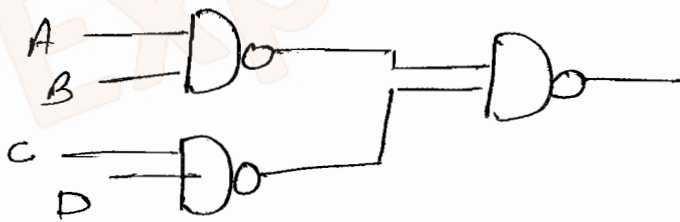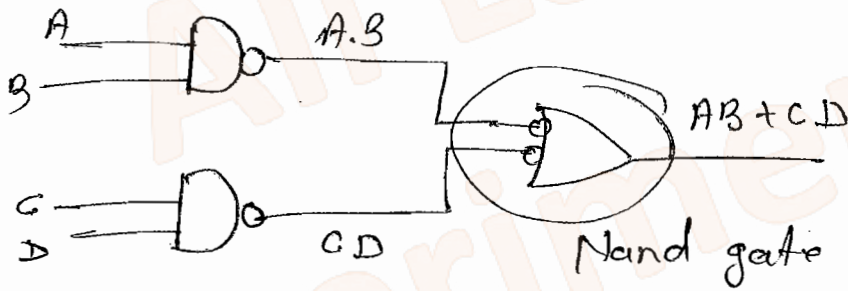


= ③

Q.




$$y = AB + CD + E$$

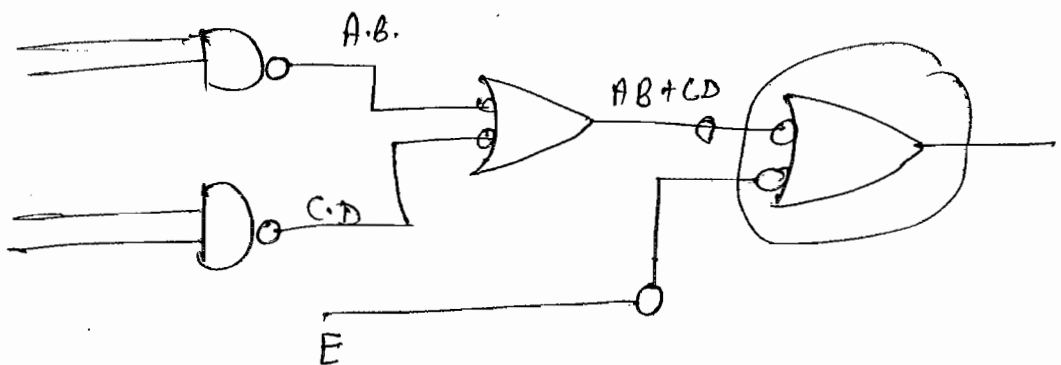

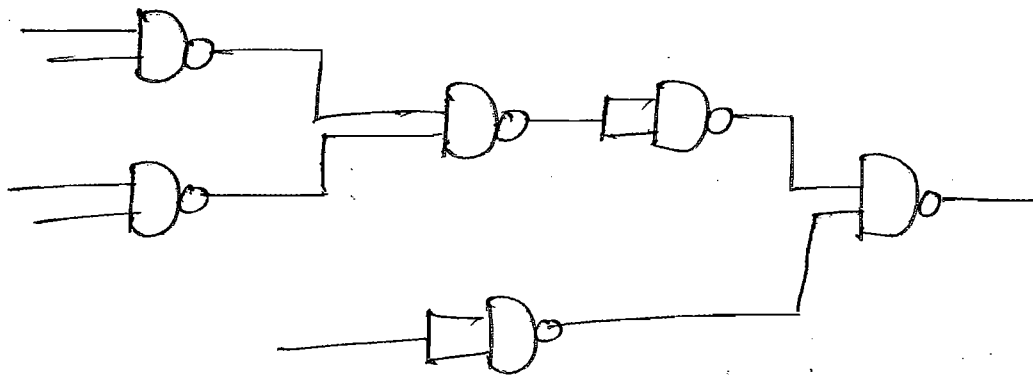



118.

$$Y = AB + CD + \bar{E}$$

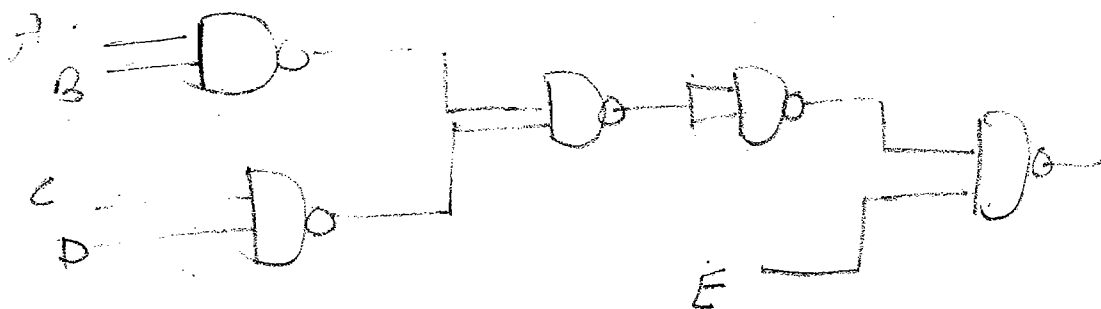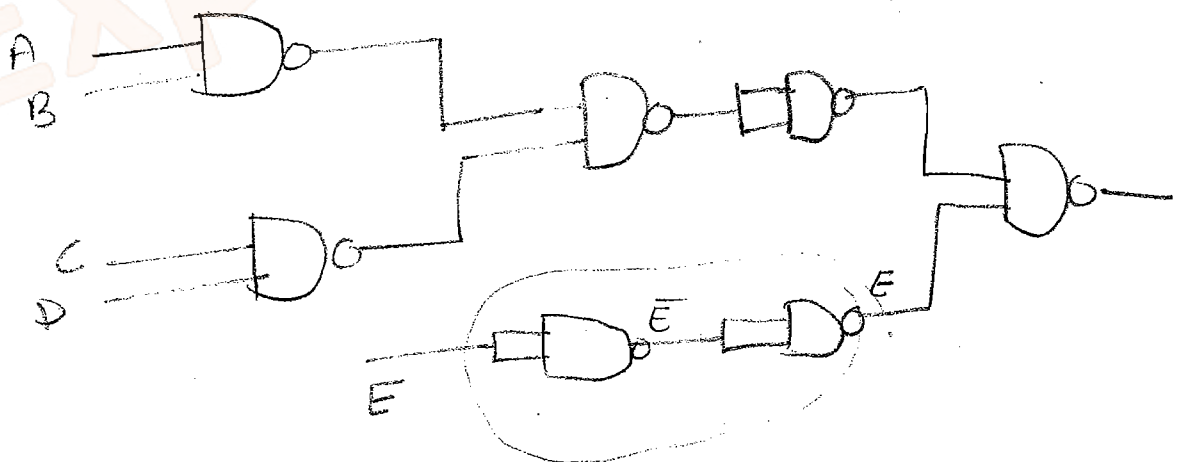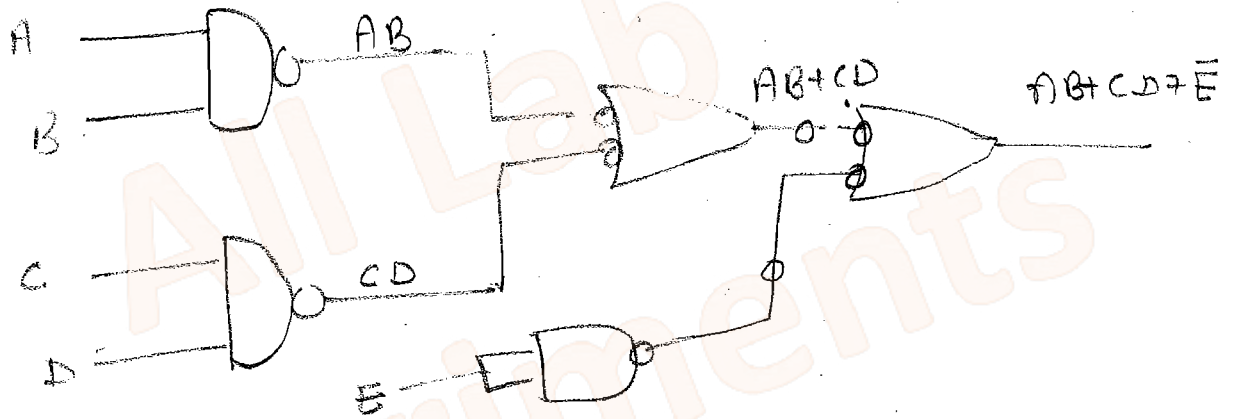


* Steps for identification minimum no. of Nor gate. \Rightarrow

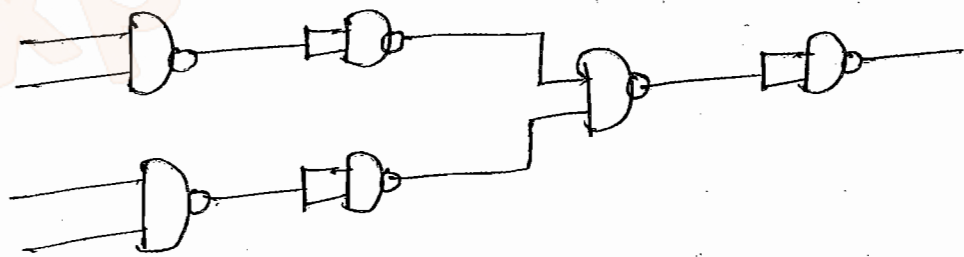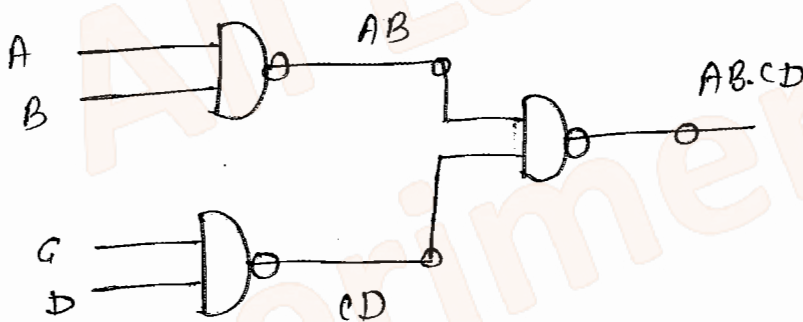- ① Draw the circuit diagram by using ordinary gates.
- ② Substitute bubble at the infront of OR-gate and at the input of AND-gate.
- ③ Replace every gate by NOR-gate it will give minimum no. of nor gate.




= 6 Ans

Q. 11

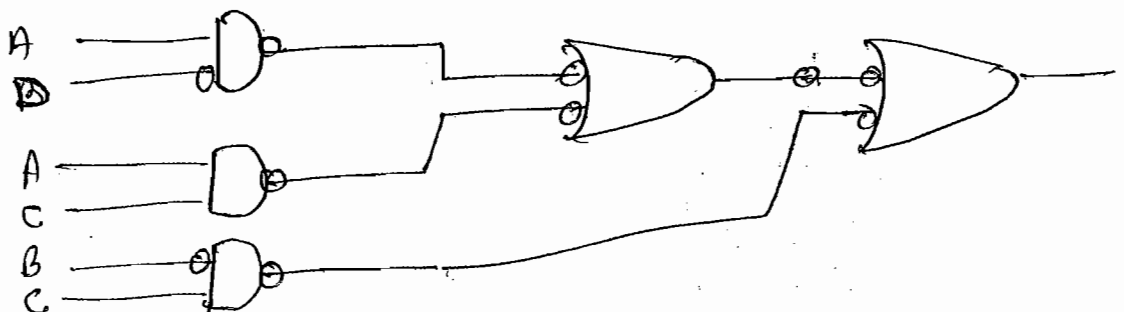

12


<https://alllabexperiments.com>

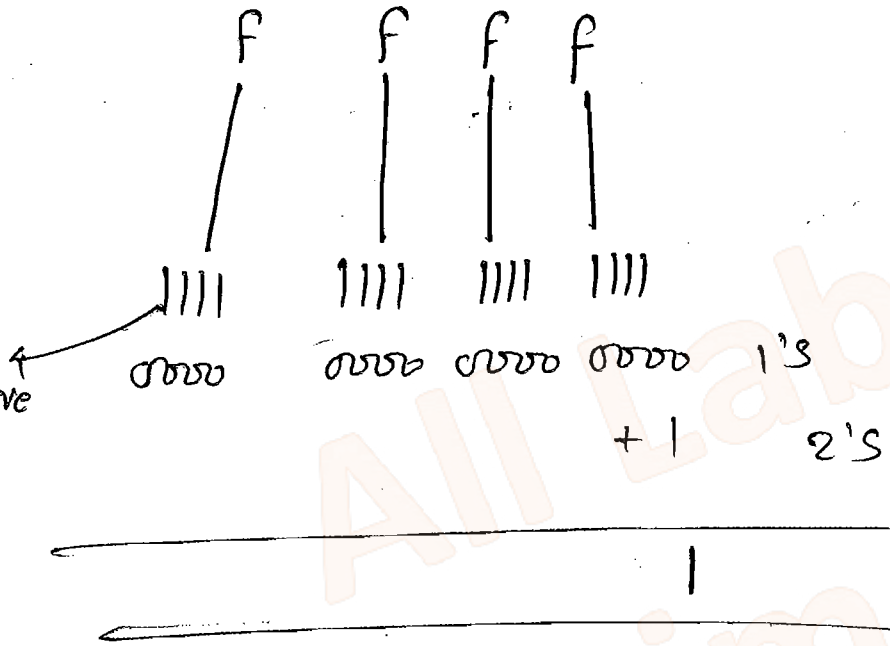

13

36	→	6	0000	
		5	0001	→ <u>Ans</u>
35		4	0010	
33		3	0011	
34		2	0100	
33		1	0101	
32	16	→	0110	
		15	0111	
		14	1000	
		13	1001	
		12	1010	
		11	1011	
		10	1100	
		9	1101	
		8	1110	
		7	1111	

14

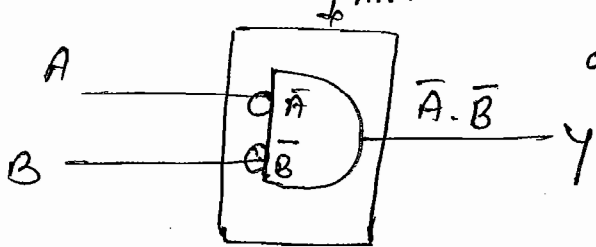

duality -

$$\overline{A} + \overline{B}$$

↑
OR

-ve logic

for +ve logic

$$Y = \overline{A} + \overline{B} \leftarrow \text{OR Gate}$$


15

$$f(A, B, C, D, E) = C + \overline{D}E$$

A	B	C	D	E
0	0	0	0	0
0	0	0	0	1
0	0	1	0	0
0	0	1	0	1
0	1	0	0	0
0	1	0	0	1
0	1	1	0	0
0	1	1	0	1
0	1	1	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1
1	1	0	0	0
1	1	0	0	1
1	1	0	1	0
1	1	0	1	1


= 4

18

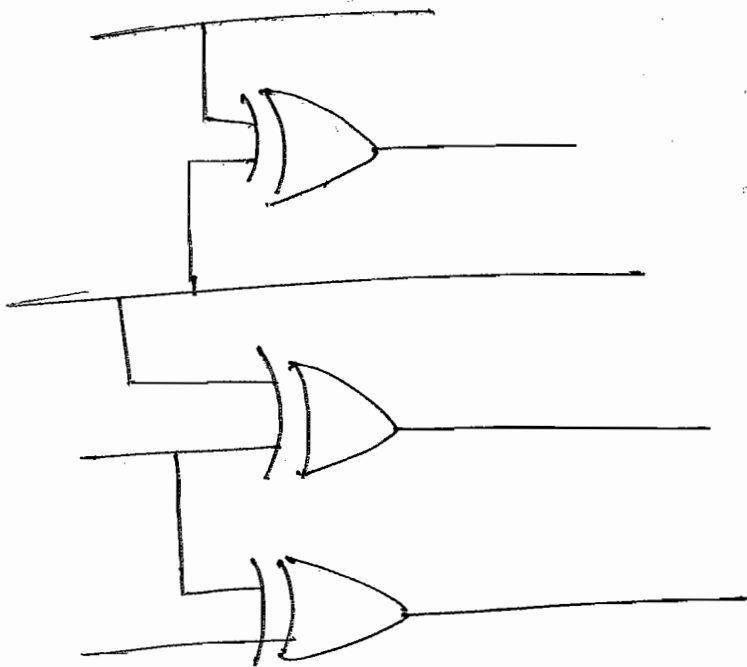

<https://alllabexperiments.com>


23

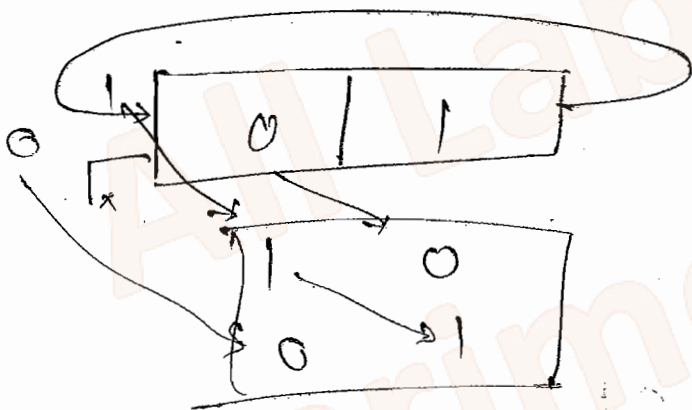

mod 2 Counter

$$4 = 2^2 = 16$$


22

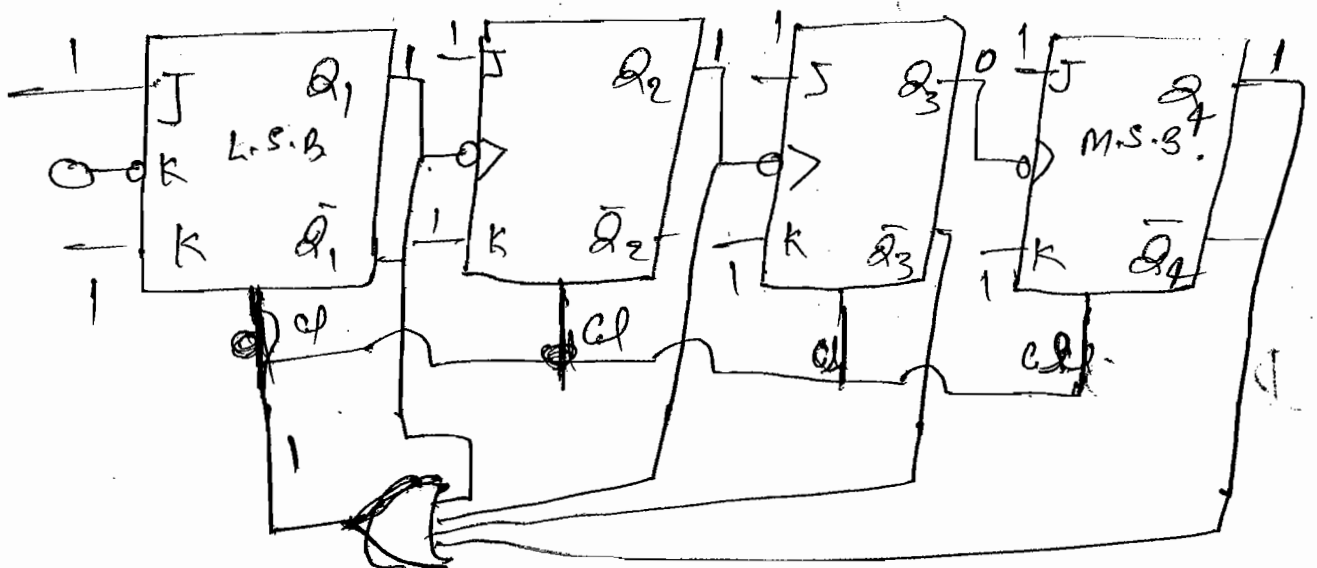

Q_4	Q_3	Q_2	Q_1
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0


1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Q. For the given circuit diagram. Identify the ~~gate~~ mod.

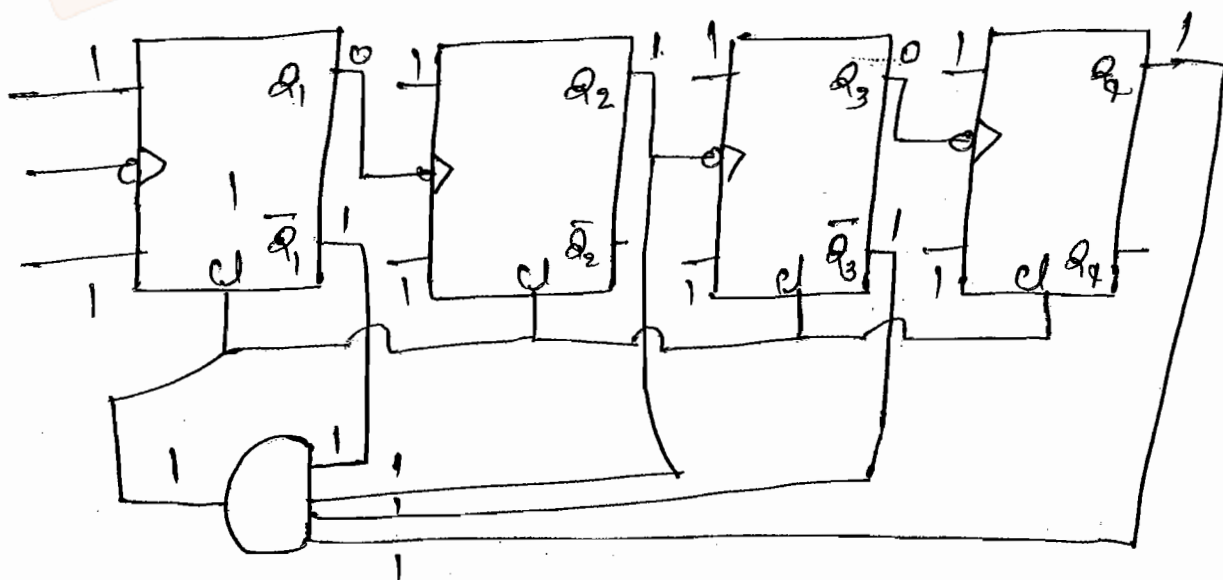


mod 10 -

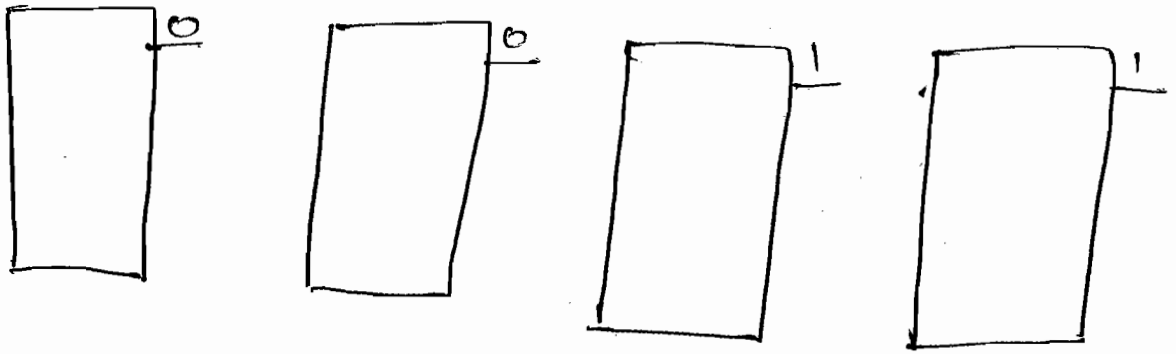Q. Draw the circuit diagram for mael - 12 up counted by using all four inputs.



<https://alllabexperiments.com> Q.18

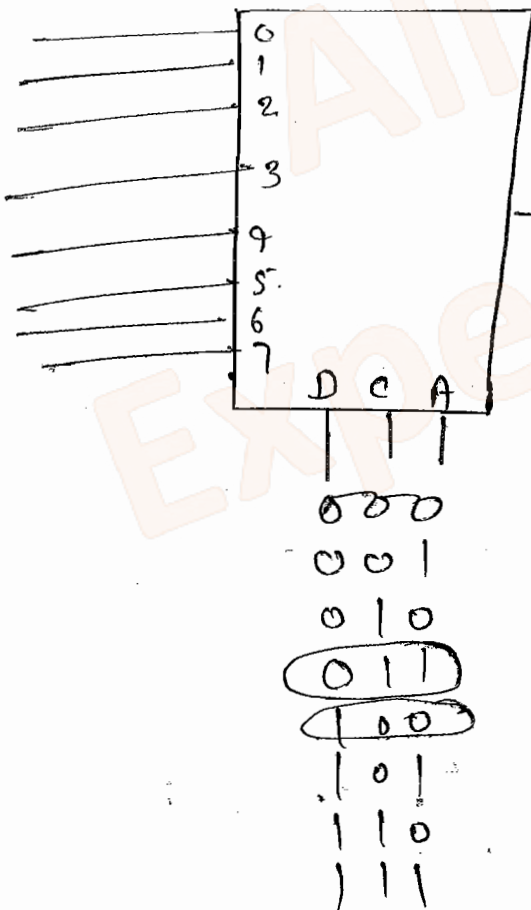



A	B	C	D	
0	0	0	0	
0	0	0	1	0
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	0
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	1
1	0	1	1	1
1	1	0	0	
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$f(A, B, C, D) = AC + A\bar{B}D + A\bar{C}D$$


	I_0	I_1	I_2	I_3	I_4	I_5
\bar{B}				1	0	0
B				1	0	1
				1	0	B

Ans

26

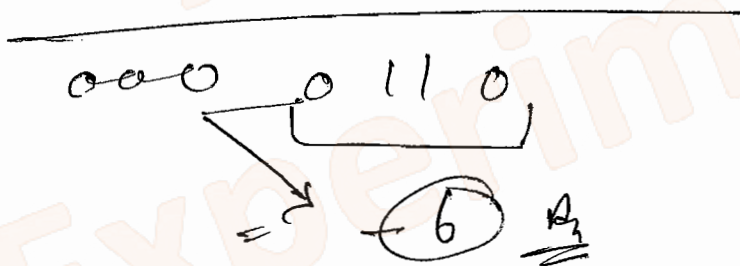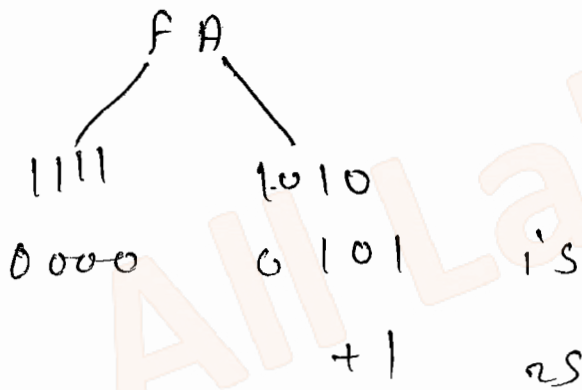

30

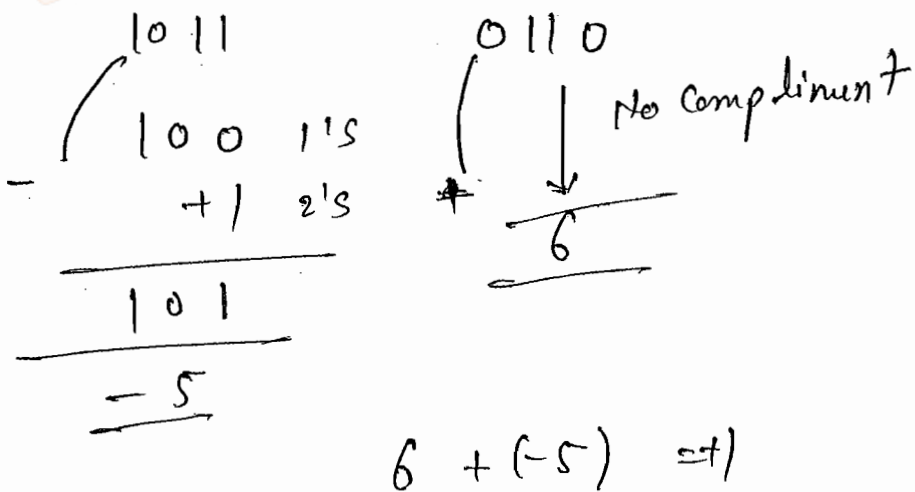

So (a) 0001

(7E)_H & (8F)_H

→ 0 111 1110
 → + 0 101 1111

0 0 1 0 0 0 0 1

EXOR

0 0 0 1 0 0 0 0

0 0 0 0 0 0 0 0


0 0 0 0 0 0 0 0 X

0 0 0 0 0 0 0 0 X X

0 0 0 0 0 0 0 0 X

0 0 1 0 0 0 0 1 X

0 0 1 0 0 0 0 1

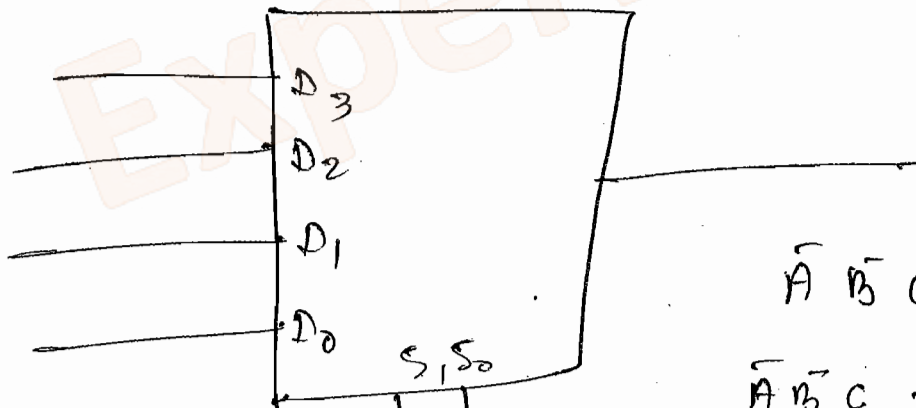

A	B
0	0
0	1
1	0
1	1

$$\bar{A} \bar{B} C + \bar{A} B + A \bar{B} + A B$$

$$\bar{A} \bar{B} C + \bar{A} B + A \bar{B} + A B$$

$$\bar{A} [B + \bar{B}C] + A [\bar{B} + B]$$

$$\bar{A} [B + C] + A$$


$$\bar{A} B + \bar{A} C + A$$

$$\bar{A} B + \bar{A} C + A$$

$$\bar{A} B + A + C$$

A + B + C

Q. 35

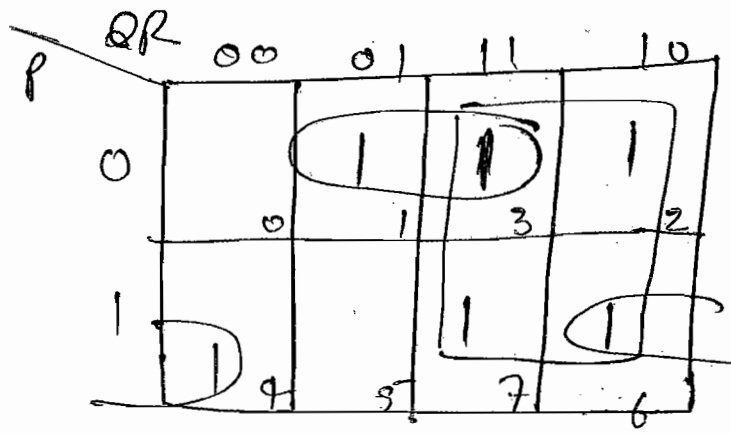


$$= \bar{P}R + P\bar{R} + Q$$

$$= P \oplus R + Q$$


one XOR and 1 OR

38) 15-bit (d)

39)

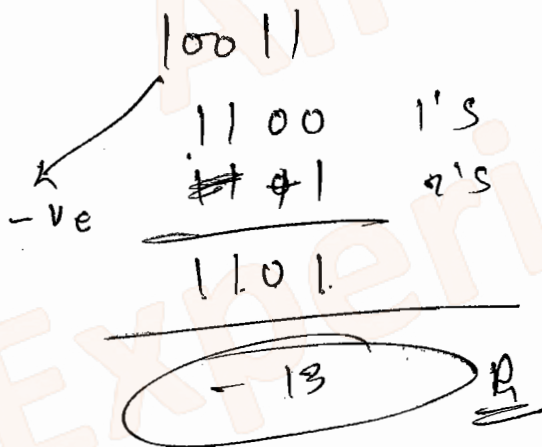


40)

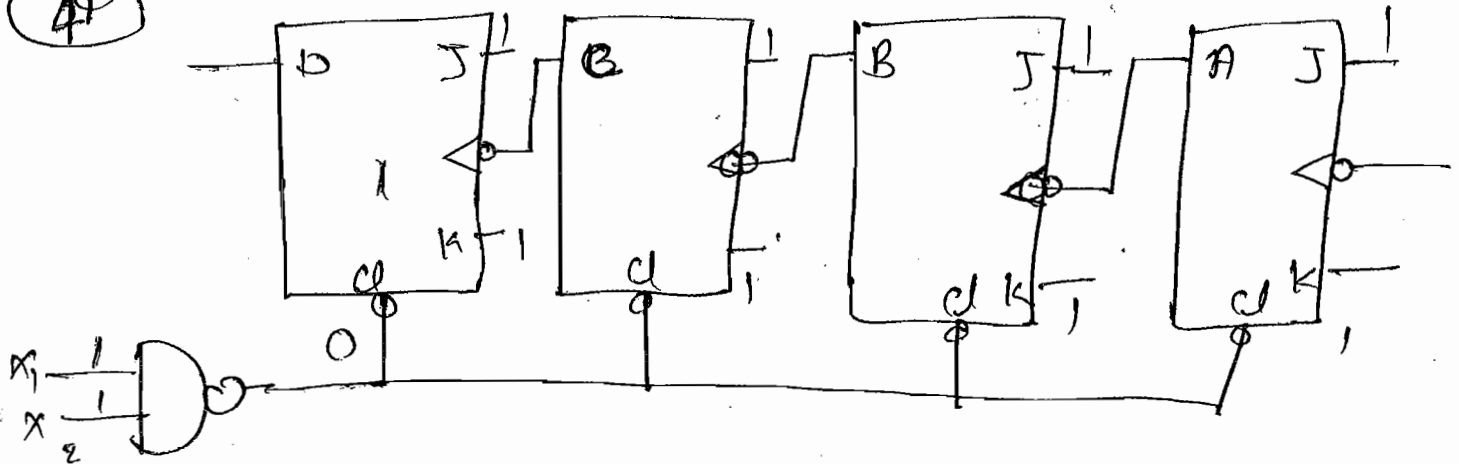

0000
 0001
 0010
 0011
 0100
 0101
 0110
 0111
 1000
 1001
 1010
 1011
 1100
 1101
 1110
 1111


46

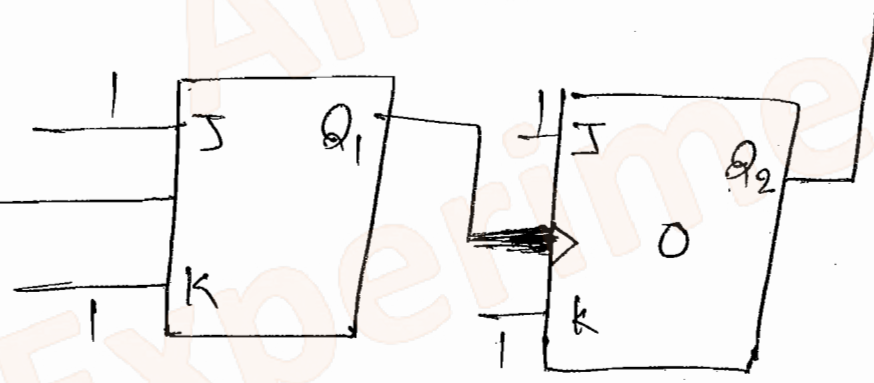

	Q_2 MSB	Q_1 LSB
4	0	0
3	0	1
2	1	0
1	1	1

← Ans


47

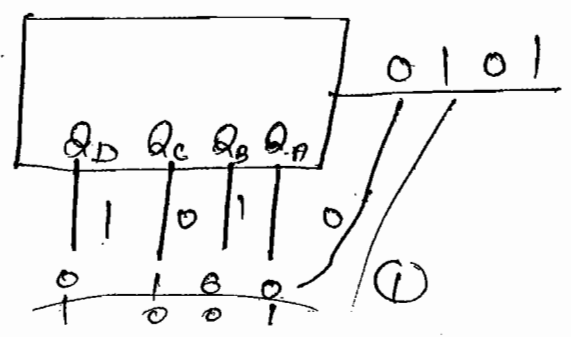

1001

* Resonance

Series RLC Network:-

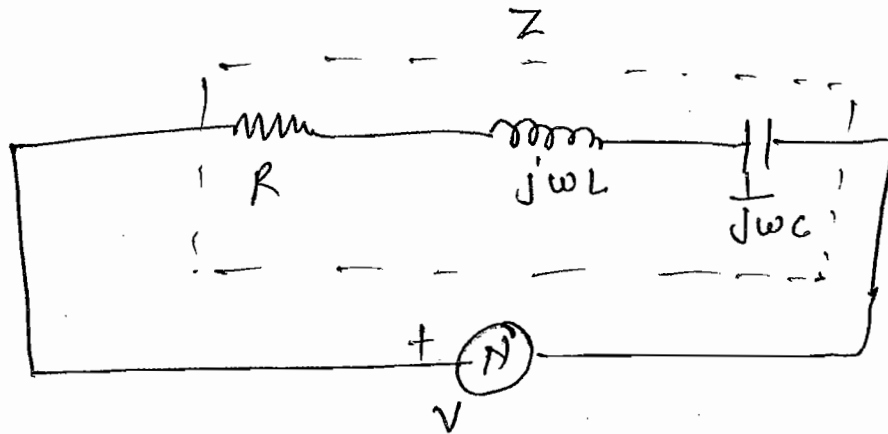

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j\omega L - \frac{1}{\omega C}$$

$$= R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

At resonance

$$\omega L = \frac{1}{\omega C}$$


$$Z = \sqrt{R^2}$$

$$\boxed{Z_{\min} = R_{\min}}$$

$$I = \frac{V}{Z}$$

$$\boxed{I = \frac{V}{R_{\min}}} \quad \leftarrow \text{maximum}$$

I_{\max} at resonance freq.

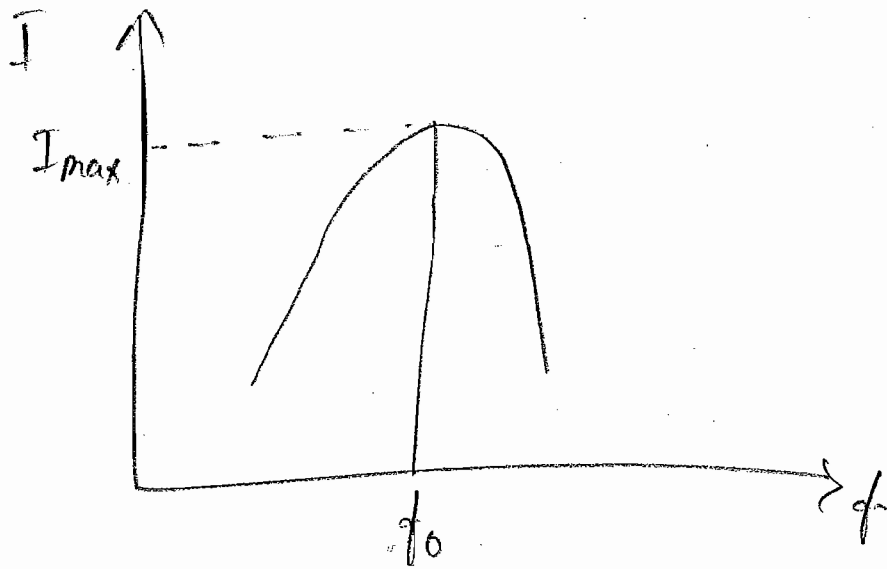


$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$

<https://alllabexperiments.com>

Use of Resonance :-

It is used to select only a single frequency by neglecting all other frequencies.


Load Speaker.
 $R = 10 \Omega$

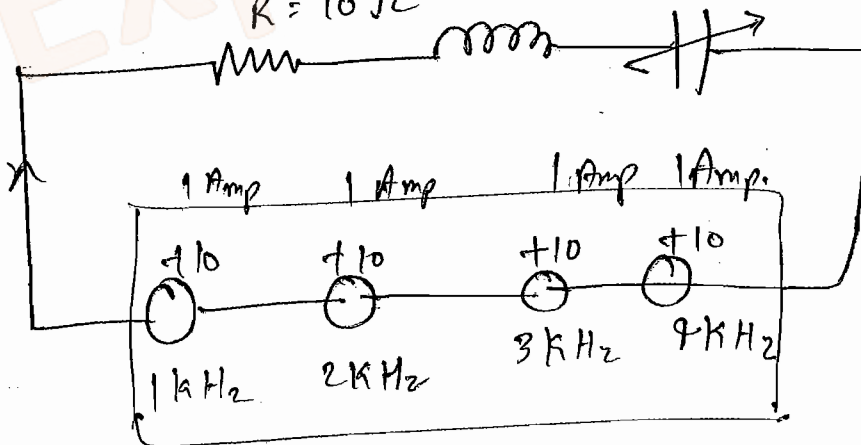

To calculate the resonance freq. of any circuit, equate imaginary component of impedance expression to zero.

Q. For the given circuit diagram determine the resonance frequency.

Solⁿ

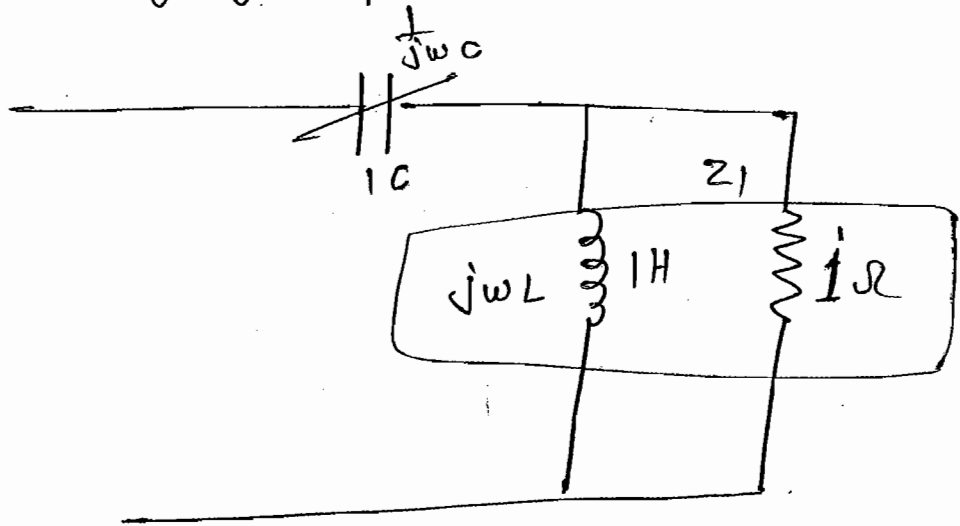

$$Z_1 = \frac{1 \times j\omega}{1 + j\omega}$$

$$\text{So } Z = Z_1 + \frac{1}{j\omega C}$$

$$= \frac{j\omega}{1 + j\omega} + \frac{1}{j\omega} = \frac{(j\omega)^2 + 1 + j\omega}{j\omega(1 + j\omega)}$$

$$= \frac{1 + j\omega - \omega^2}{j\omega(1 + j\omega)}$$

$$= \frac{-j(1 - \omega^2) + j\omega}{\omega(1 + j\omega)}$$

$$= \frac{-j(1 - \omega^2) + j\omega(1 - j\omega)}{\omega(1 + j\omega)(1 - j\omega)}$$

$$= \frac{j[(1 - \omega^2) + j\omega - j\omega(1 - \omega^2) + \omega^2]}{\omega(1 + \omega^2)}$$


$$\begin{aligned}
 &= \frac{-j(1-\omega^2) + \omega - \omega(1-\omega^2) - j\omega^2}{\omega(1+\omega^2)} \\
 &= \frac{\omega - \omega(1-\omega^2) - j[1-\omega^2 + \omega^2]}{\omega(1+\omega^2)} \\
 &= \frac{\omega - \omega(1-\omega^2) - j}{\omega(1+\omega^2)} \\
 &= \frac{\omega - \omega(1-\omega^2)}{\omega(1+\omega^2)} - \frac{j}{\omega(1+\omega^2)}
 \end{aligned}$$

$$\text{So } \frac{-1}{\omega(1+\omega^2)} = 0$$

$-1 \neq 0$ not possible

So resonant freq. does not exist.

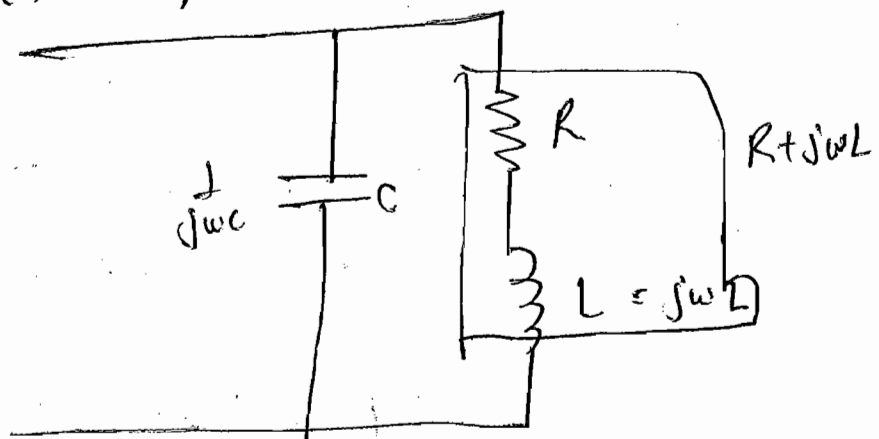11. For the given circuit diagram calculate given frequency. (Resonance).



for simplicity

$$\text{Conductance} = j\omega C + \frac{1}{R + j\omega L} \quad (1)$$

$$= \frac{j\omega c [R + j\omega L] + 1}{(R + j\omega L)(R - j\omega L)}$$

$$= \frac{[j\omega c [R + j\omega L] + 1] [R - j\omega L]}{R^2 + \omega^2 L^2}$$

$$= \frac{j\omega R c [R + j\omega L] + R + \omega^2 L c (1 + j\omega L) - j\omega}{(R^2 + \omega^2 L^2)}$$

$$= \frac{j\omega R^2 c - \omega^2 R c + R + \omega^2 R L c + j\omega^2 L^2 c - j\omega}{R^2 + (\omega L)^2}$$

equating imaginary part to zero.

$$\frac{j[\omega R^2 c + \omega^2 L^2 c - \omega L]}{R^2 + (\omega L)^2} = 0$$

$$\frac{R^2 c + \omega^2 L^2 c - L}{R^2 + (\omega L)^2} = 0$$

$$R^2 c + \omega^2 L^2 c - L = 0$$

$$\omega^2 L^2 c = L - R^2 c$$


$$\omega^2 = \frac{L - R^2 c}{L^2 c}$$

$$\omega = \sqrt{\frac{1}{Lc} - \frac{R^2}{L^2}}$$

Ans

Q. Calculate the resonance freq.

- (a) 1.41
- (b) 1
- (c) 2
- (d) 1.73

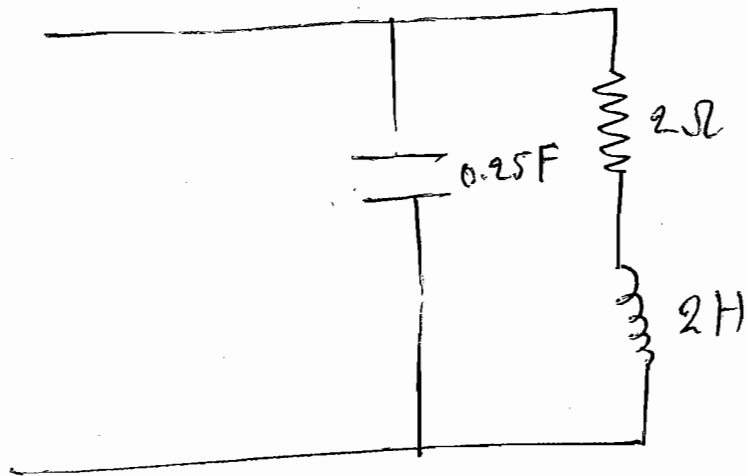

Normal $\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \times 0.25}} = 1.41$

But it is not right



$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{C^2}} = 1$

Solⁿ


<https://alllabexperiments.com>

Digital



68

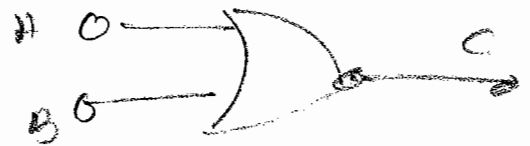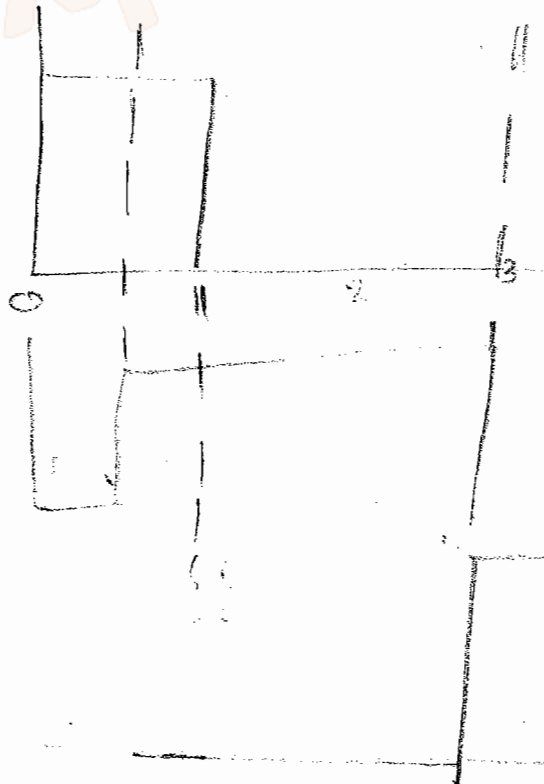

Q1

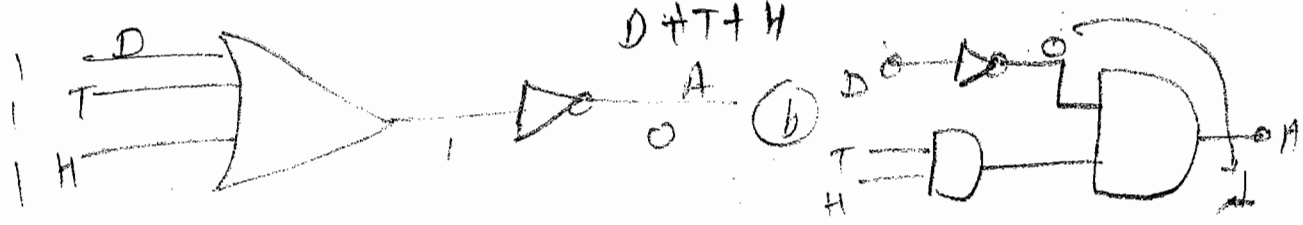

Q2

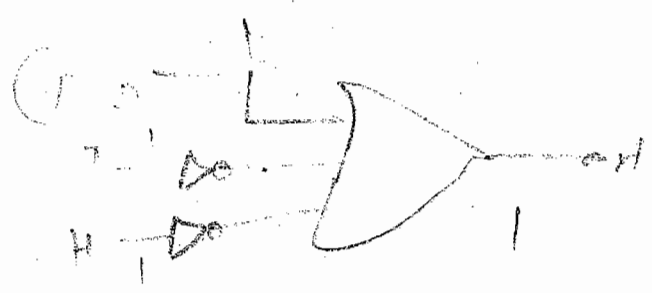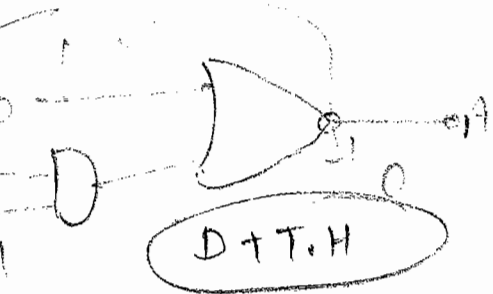

T → 1, < a

H → 1, < a

D = 1 ← one the clear

D as T and humidity

1 1 1 → A = 0


D + T.H

A = 0

Q2 a


All Lab Experiments

* Half - Wave Rectifier :-

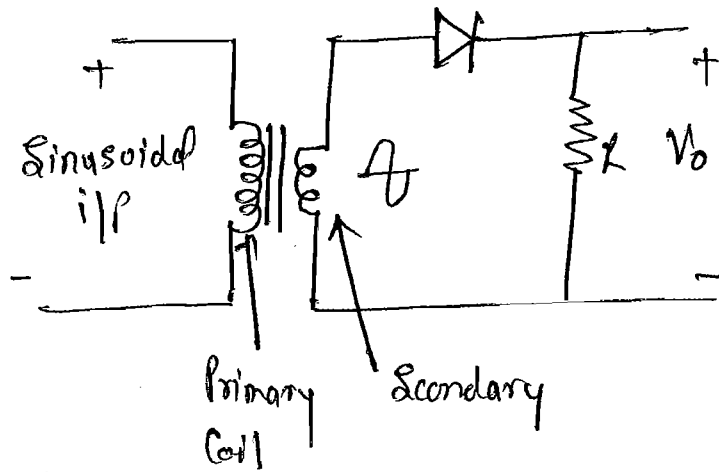

Step-up transformer increases the amplitude of applied i_p and reproduces at secondary of the transformer.

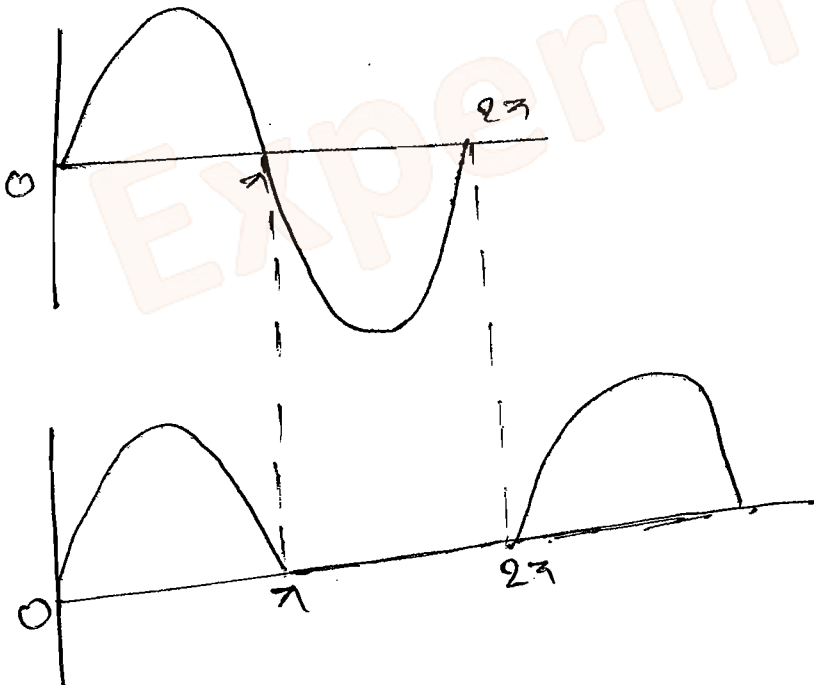If the applied i_p whose amplitude is decrease, it called as step down transformer.



* D.C. Value or Average value :-

$$= \frac{1}{2\pi} \int_0^{2\pi} f(x) dx$$

$$= \frac{1}{2\pi} \int_0^{\pi} V_m \sin(x) dx$$